

# **POWER ELECTRONICS LAB**

**EE 536**

**EXPERIMENTS MANUAL**

## **SAFETY INFORMATION**

- Laboratory work always entails a higher risk of accidents.
- The device may only be operated by persons who are in a position to recognize shock hazards and to implement the proper safety measures.
- If measurements are to be made where there is a shock hazard, **IT IS NOT PERMITTED TO WORK ALONE**: a second person must be informed.
- In accordance with the IEC regulations, metal parts not carrying a voltage in normal operation (e.g. housings) are to be connected to the PE ground conductor. The ground conductor is provided solely for this purpose and may not be connected with the neutral conductor, N, of the circuit!
- Always use safety connecting leads.
- Do not switch on the power mains until the circuitry has been carefully checked
- The mains voltage must be disconnected before intervening in the experiment set-up and making any changes or additions to circuitry.

## EXPERIMENT ONE

### UNCONTROLLED RECTIFIERS

#### INTRODUCTION

Static rectifiers with diodes perform the basic function of dc rectification: the output voltage of a rectifier is a pulsating unipolar voltage with an average value. The common type of an ac/dc converter is composed by a transformer and a diode rectifier circuit, as shown in Fig.1.

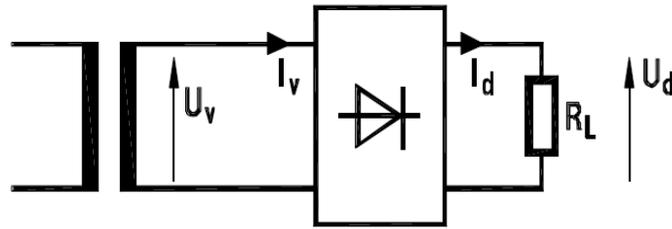


Fig. 1 AC/DC uncontrolled rectifier

In considering rectifier circuits it is important to know the relationships between the input (rms values) and output (average values) parameters, which are:

$U_v$  = alternating line voltage (r.m.s.)

$I_v$  = alternating line current (r.m.s.)

$U_d$  = output dc voltage

$I_d$  = output dc current

#### SINGLE PULSE RECTIFIER

The single pulse rectifier, or half wave rectifier of Fig.2, represents the simplest form of a static ac/dc converter.

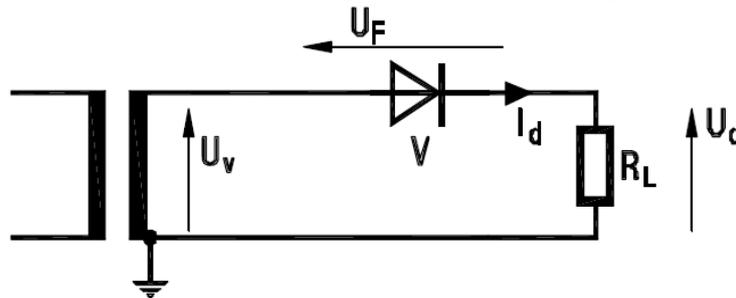


Fig. 2 Half wave uncontrolled rectifier, ohmic load

When an ohmic load  $R$  is applied, the diode switches the positive half of the ac voltage  $U_v$  to the load and blocks the negative half-wave. As a result, the dc voltage  $U_d$  is made up of intermittent (discontinuous) sinusoidal half-waves: the direct current  $I_d$  follows the same sinusoidal time profile as the dc voltage and is in phase with the latter, as illustrated in the following Fig.3.

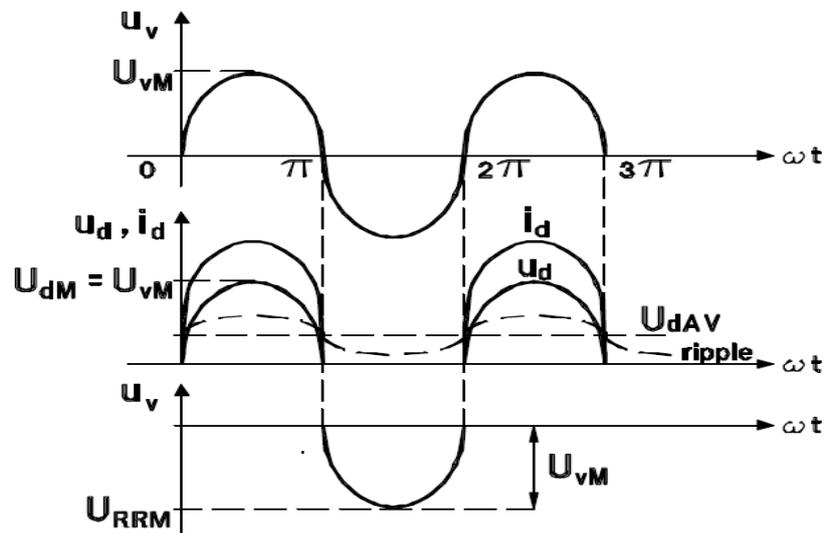


Fig. 3 Voltage and current waveforms, half-wave uncontrolled rectifier, ohmic load

All the following formulae apply to resistive load, neglecting losses in the rectifier.

Average value of output voltage  $U_{dAV} = 0.45U_V$

Rms value of output voltage  $U_{dRMS} = 0.707U_V$

Form factor of output voltage  $f = U_{dRMS}/U_{dAV} = 1.57$

Ripple factor  $w = 100(f^2-1)^{0.5} = 121\%$

Repetitive peak reverse voltage value of the diode  $U_{RRM} = U_{VM} = 1.414U_V$

### **Inductive and ohmic-inductive loads**

If we examine the theoretical load case of a purely inductive load, the diode conducts at the positive zero transition of the ac voltage  $U_V$  and the current  $I_d$  increases continuously: the choke stores magnetic energy. At the next zero transition with negative ac voltage, the direct current continues to flow at a decreasing rate until the choke has been discharged: since there are no resistive losses, the discharge time equals the charging time and the current conduction time equals the cycle duration  $T$  of the ac voltage.



If we now consider the real case of an ohmic-inductive R-L series load, the current conduction time varies between  $T/2$  and  $T$ , depending on the magnitude of  $R$  and  $L$ . More details can be found in the theoretical part of the next Experiment when controlled rectifiers are discussed.

# SINGLE-PULSE UNCONTROLLED RECTIFIER, OHMIC-INDUCTIVE LOAD

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

Circuit diagram

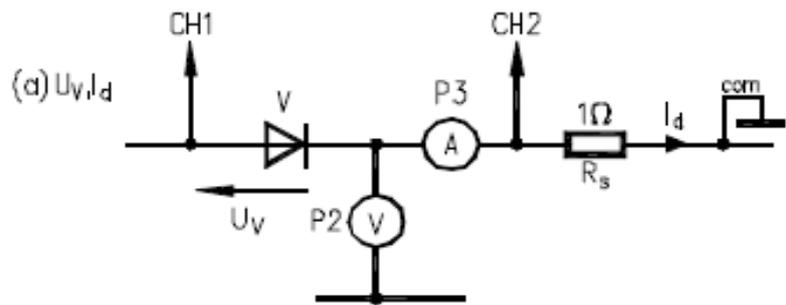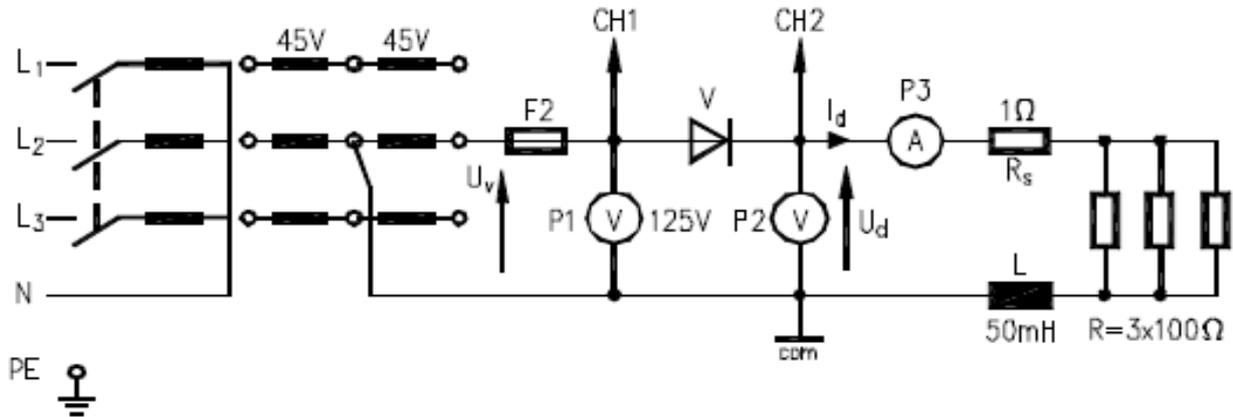

### Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding detail (a) at first.

#### 1) Voltage and current measurements

Supply the circuit and measure:

1.1) the rms value  $U_v$  of the supply voltage by the voltmeter P1;

1.2) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the output voltage by the voltmeter P2;

1.3) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the output current by the ammeter P3.

Enter the measured value in the following table.

$U_v$ (V)	$U_{dAV}$ (V)	$U_{dRMS}$ (V)	$I_{dAV}$ (A)	$I_{dRMS}$ (A)

Evaluate the following characteristic data of the rectifier

Form factor =

Ripple factor =

#### 2) Recording on the oscilloscope

##### Note

*Since the basic instrument set does not normally allow simultaneous measurements, the measures may have to be carried out successively.*

2.1) Recording the supply  $U_v$  and direct  $U_d$  voltages.

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 (voltage  $U_v$ )

Channel 2 (voltage  $U_d$ )

2.2) Recording the voltage  $U_v$  and the output current  $I_d$ .

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

Channel 1 ( $U_v$  voltage)

Channel 2 (current  $I_d$  proportional to voltage at shunt  $R_s = 1 \Omega$ ): 0.5 V/div

3) Repeat steps (1) and (2) above for  $L = 100$  mH and  $L = 125$  mH

4) Compare measurements with the expected theoretical values.

## EXPERIMENT TWO

### SINGLE-PULSE THYRISTOR-CONTROLLED CONVERTER

#### INTRODUCTION

The single-pulse converter is the simplest form of controlled rectifier circuits, as shown in Fig. 1.

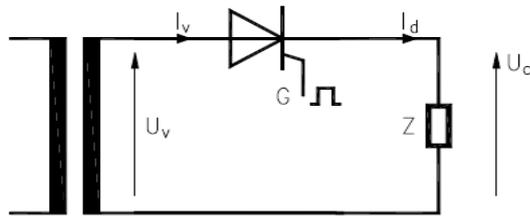


Fig.1 Single-pulse converter

In practical power electronics this power converter is of little importance on account of the high ripple of the dc voltage. Nevertheless, this converter will be investigated since the resultant knowledge is of fundamental importance in understanding converters with higher pulse numbers.

#### Single-pulse converter with ohmic load

Ohmic load represents the simplest and most easily described load variant for a rectifier since the characteristic curves for a voltage and current at the ohmic load are identical in time and phase.

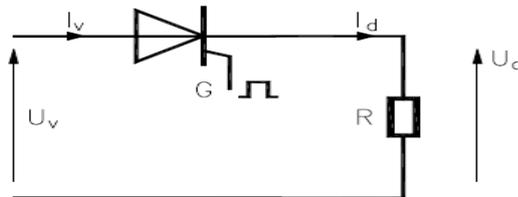


Fig.2 Converter with ohmic load

With no trigger pulses the silicon controlled rectifier (SCR), or thyristor, is in off state and the current cannot flow. When the anode voltage is positive the SCR is triggered after a delay controlled by the gate angle  $\alpha$ : the current flows in the load until the current again drops to zero when the feed voltage crosses zero and the SCR blocks. The gate angle  $\alpha$  can be controlled from  $0^\circ$  to  $180^\circ$  and the conducting angle is  $(\Theta = 180^\circ - \alpha)$ . The voltage and current time profiles are illustrated in Fig.3. Note that  $\alpha = 0^\circ$  corresponds to diode case (uncontrolled rectifier).

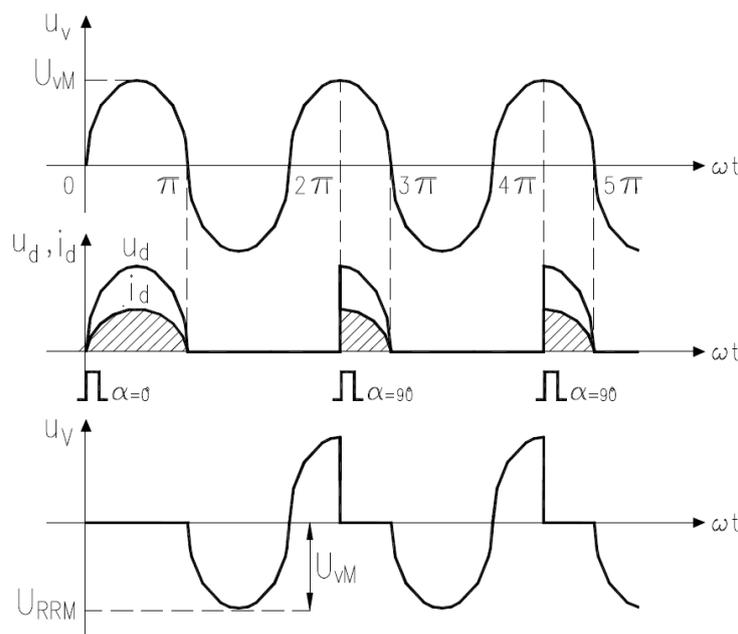


Fig.3 Voltage and current time profiles of the single pulse converter with ohmic load

All the following formulae apply to resistive load, neglecting losses in the converter.

Assuming that  $U_{dAVo} = U_{vM}/\pi$  and  $U_{dRMSo} = U_{vM}/2$  are the average and rms values for the gate angle  $\alpha=0^\circ$ .

Average value of output voltage  $U_{dAV} = 0.5(1+\cos\alpha)U_{dAVo}$

Rms value of output voltage  $U_{dRMS} = U_{dRMSo}[1-(\alpha/\pi)+[\sin(2\alpha)/(2\pi)]]^{0.5}$

Form factor of output voltage  $f = U_{dRMS}/U_{dAV}$

Ripple factor  $w = 100(f^2-1)^{0.5}$

**Single-pulse converter with inductive load**

The purely inductive load represents an ideal load; in practice the choke coil has an ohmic dissipative resistance which cannot be disregarded.

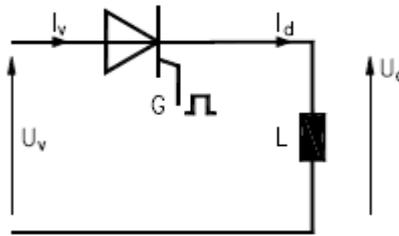


Fig.4 Converter with inductive load

As in circuit with ohmic load, the SCR can be triggered when the anode voltage is positive.

According to law of induction, the load current varies continuously and not abruptly as in the case of an ohmic load. During the positive voltage half-cycle, magnetic energy is stored in the inductance; when the feed voltage crosses zero the load current continues to flow until the inductance has been discharged. The gate angle  $\alpha$  can be controlled from  $0^\circ$  to  $180^\circ$  while the conducting angle is  $\Theta = 2(180^\circ - \alpha)$ . The voltage and current time profiles are illustrated in Fig.5. Note that  $\alpha = 0^\circ$  corresponds to diode case (uncontrolled rectifier).

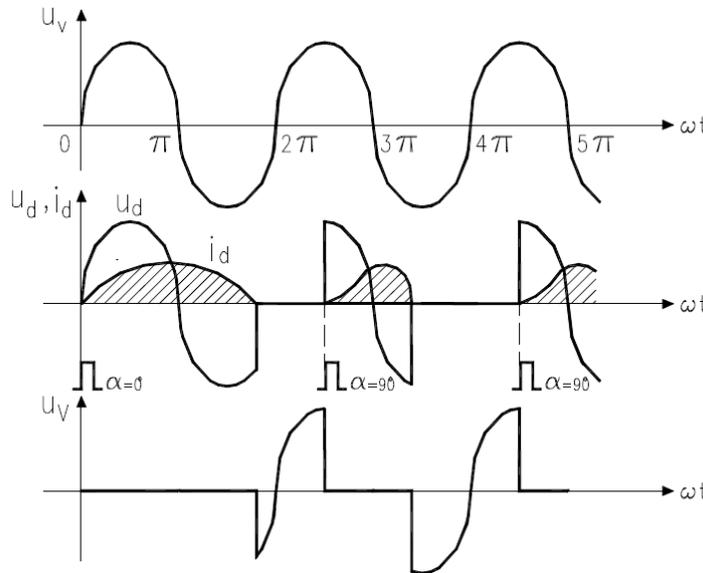


Fig.5 Voltage and current time profiles with inductive load

**Single-pulse converter with series ohmic-inductive load**

Circuits containing R and L in series are a load type frequently found in practice.

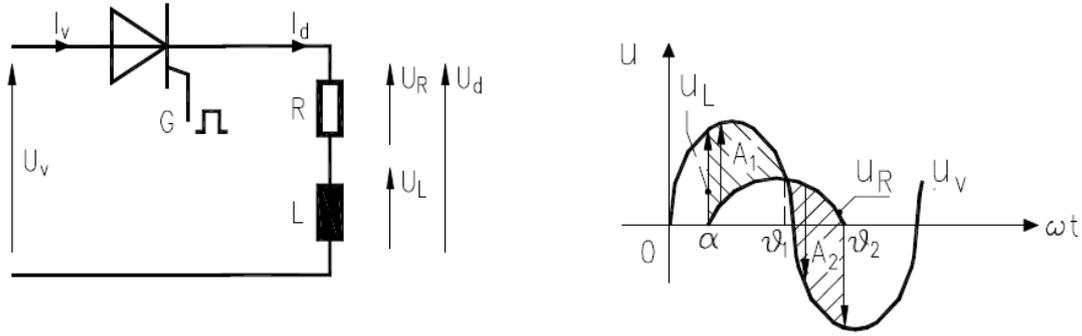


Fig.6 Converter with series ohmic-inductive load

Once again the inductance prevents any abrupt load current changes. When the SCR is fired on at  $\alpha$  control angle during the positive half-cycle of voltage  $u_v$ , the current begins to flow.

During  $\alpha$  to  $\vartheta_1$ , the voltage  $u_L = u_v - u_R$  is positive and the current increases; beyond  $\vartheta_1$ ,  $u_L$  becomes negative and the current begins to decline and becomes zero at  $\omega t = \vartheta_2$  corresponding to area  $A_1 = \text{area } A_2$ . The direct current time profile is made up of a sinusoidal current which lags behind the  $u_v$  voltage by the load phase angle  $\varphi = \arctan(\omega L/R)$  and the equalizing current decaying with time constant  $\tau = L/R$ : at firing point the value of equalizing current is opposite and equal to sinusoidal current value. Since the direct current continues to flow as a result of the storage capacity of the inductance when the feed voltage crosses zero, the direct voltage time profile is made up of positive and negative areas: the negative area reduces the mean value.

The gate angle  $\alpha$  can be controlled from  $0^\circ$  to  $180^\circ$  while the conducting angle  $\Theta$  lies between  $(180^\circ - \alpha)$  and  $2(180^\circ - \alpha)$ . The direct current decreases constantly as the gate angle  $\alpha$  increases and when  $\alpha = 180^\circ$  the  $I_{dAV}$  and  $I_{dRMS}$  values are zero. The voltage and current time profiles are illustrated in Fig. 7

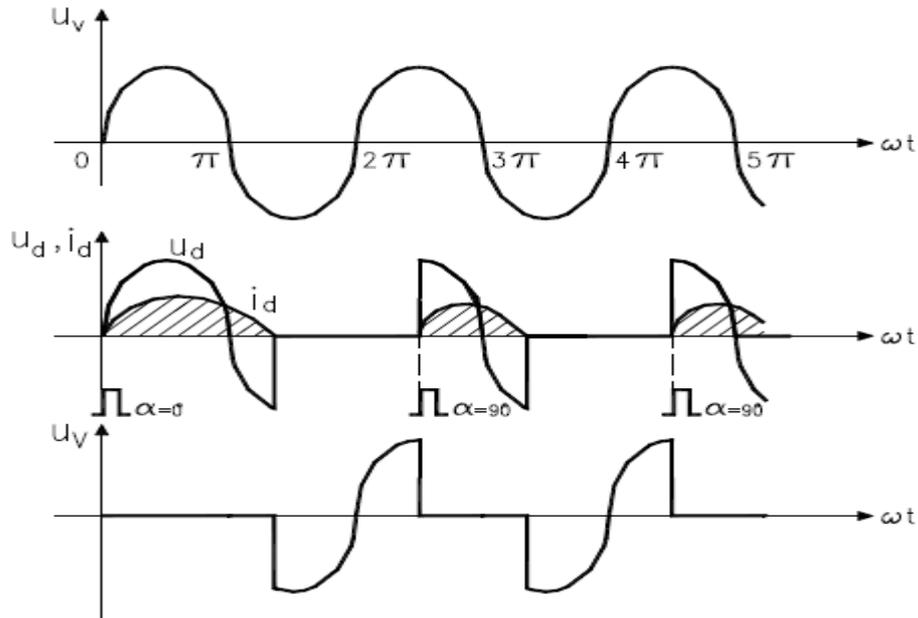


Fig. 7 Voltage and current time profiles with series R-L load

Assuming no energy is initially stored in the inductor, the load current can be expressed as

$$i_d = (U_{vM}/Z)[\sin(\omega t - \phi + \alpha) + \sin(\phi - \alpha)e^{-(t/\tau)}]$$

Where  $Z = [R^2 + (\omega L)^2]^{0.5}$

To find the average value of output voltage, conduction angle,  $\theta$  should be first determined, then use

$$U_{dAV} = (0.5U_{vM}/\pi)[\cos \alpha - \cos(\alpha + \theta)]$$

### Single-pulse converter with free-wheeling diode and ohmic-inductive load

To avoid that with ohmic-inductive load the voltage negative areas reduce the mean value of the load voltage a free-wheeling diode  $V_F$  is connected in parallel to the load and its polarity is such that it turns off when the voltage  $U_d$  is positive.

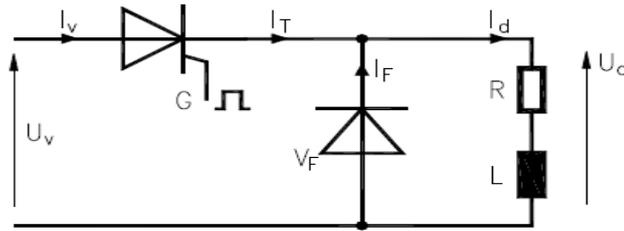


Fig.8 Converter with free-wheeling diode

When the feed voltage crosses the zero, the free-wheeling diode  $V_F$  continuously conducts the inductive current without return of energy into ac supply and fixes the load negative voltage at about 1V until the magnetic energy stored in the inductance has been discharged with time constant  $\tau = L/R$ . Since there are no negative components the mean value of direct voltage is the same as that in the case of an ohmic load. As a result, free-wheeling diode prevents negative voltage areas and thus the return of energy from the load to the ac supply while if the inductance is sufficiently large a non-intermittent (continuous) load current flows. The voltage and current time profiles with intermittent (discontinuous) conduction are illustrated below.

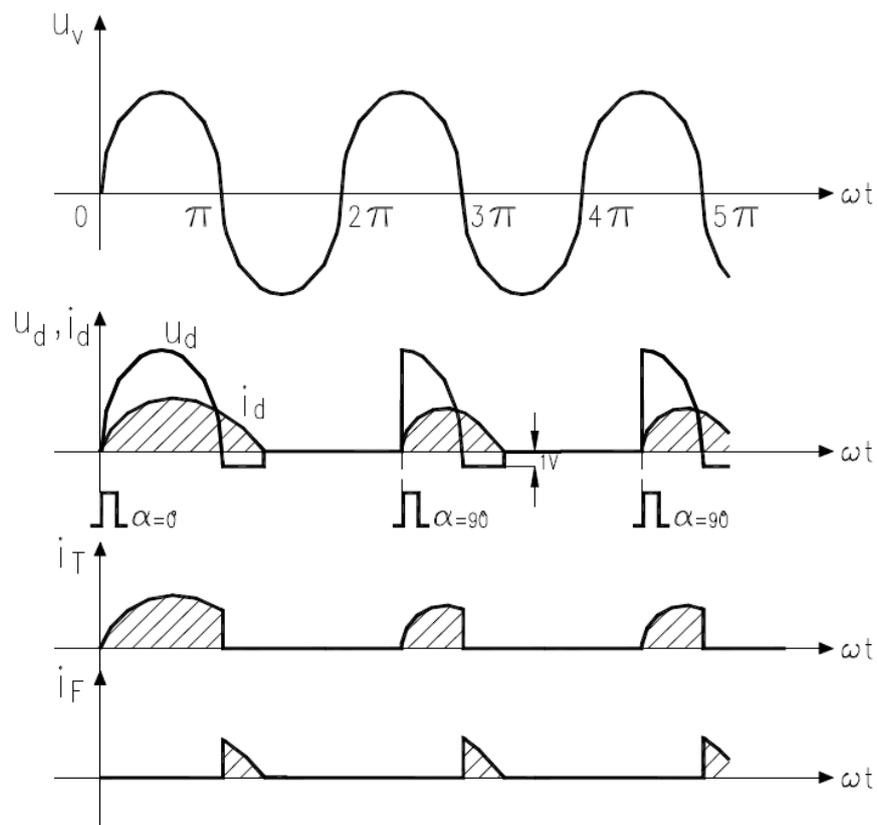


Fig.9 Voltage and current time profiles, Ohmic-inductive load and free-wheeling diode, intermittent (discontinuous) conduction

For both ohmic and ohmic-inductive loads the average value of output voltage, assuming lossless circuit can be expressed as



$$U_{dAV} = (0.5U_{vM}/\pi)(1 + \cos \alpha)$$

# SINGLE-PULSE CONTROLLED CONVERTER, OHMIC-INDUCTIVE LOAD

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

Circuit diagram

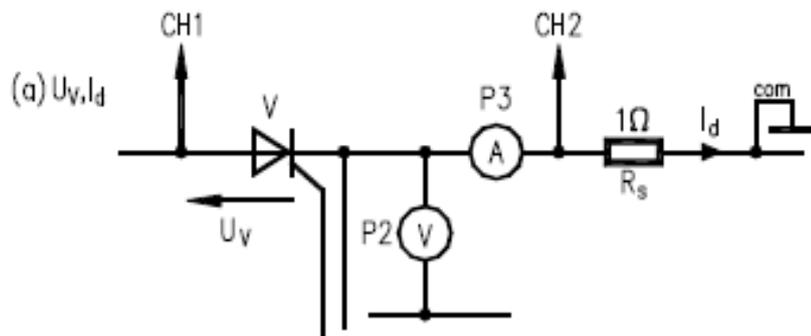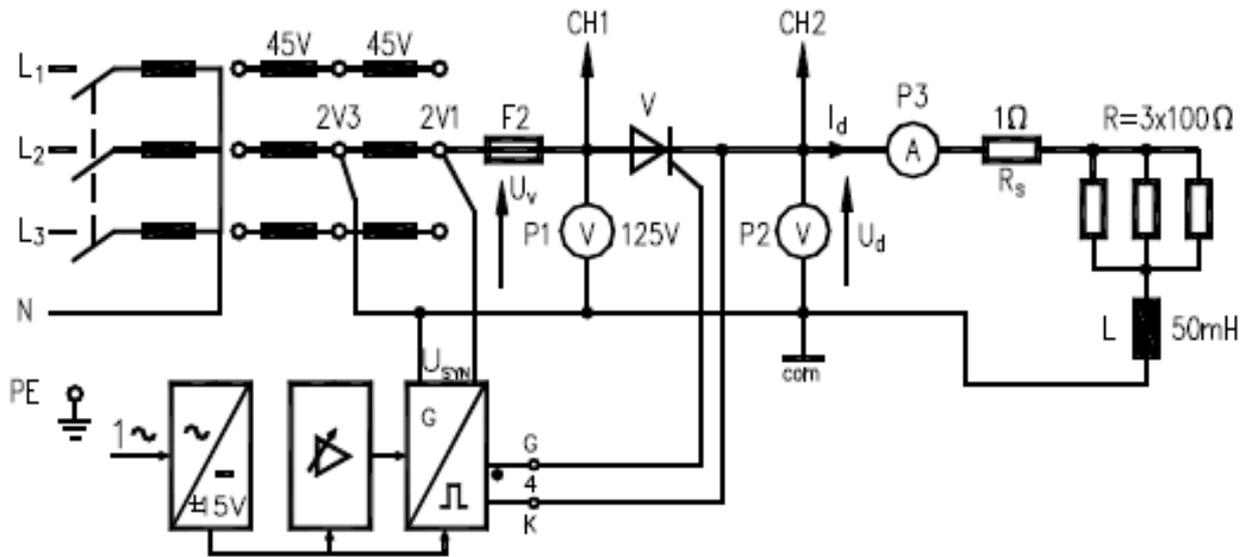

**Experiment procedure**

Assemble the circuit according with the foregoing topographic diagram, disregarding detail (a) at first.

1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V1/2V3 of the transformer.

Connect the pulse transformer 4 to gate/cathode circuit of the SCR: socket marked with a dot to the gate.

2) Basic settings

2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 10 V.

2.2) Control unit DL2616

Control angle  $\alpha_o$  switch on 0° position.

“Pulse shape” switch on pulse train position.

Inhibit voltage UINH = 15 V (open).

3) Voltage and current measurements

Supply the circuit and measure:

3.1) the rms value  $U_v$  of the supply voltage by the voltmeter P1;

3.2) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the load voltage by the voltmeter P2;

3.3) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the load current by the ammeter P3.

Enter the measured value as a function of the gate angle  $\alpha$  in the table below.

**HINT**

*In order to set the gate angle, set only a half-wave of the direct voltage with the width of 9 (or 6) grid divisions on the oscilloscope: each division then corresponds to an angle of 20° (or 30°).*

*Another system is the use of phase shift  $a_o$  in the control unit:*

*1) Set  $\alpha_o = 0^\circ$  and  $U_c = 10$  V to obtain the firing angle  $\alpha = 0^\circ$  and carry out the measurements.*

*2) Set now  $\alpha_o = 30^\circ$  to obtain the firing angle  $\alpha = 30^\circ$  and, for example, note down the  $I_{dRMS30}$  value.*

*3) Set again  $\alpha_o = 0^\circ$  and adjust  $U_c$  in order to obtain  $I_{dRMS30}$  and now set again  $\alpha_o = 30^\circ$  in order to obtain the firing angle  $\alpha = 60^\circ$ : note down  $I_{dRMS60}$ .*

*4) Set again  $\alpha_o = 0^\circ$  and adjust  $U_c$  in order to obtain  $I_{dRMS60}$  and now set again  $\alpha_o = 30^\circ$  in order to obtain the firing angle  $\alpha = 90^\circ$  and so on.*

$U_v =$

$\alpha$ (°)	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$	$\alpha_5$	$\alpha_6$	$\alpha_7$
$U_{dAV}$ (V)								
$U_{dRMS}$ (V)								
$I_{dAV}$ (A)								
$I_{dRMS}$ (A)								

$\alpha$ (°)	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$	$\alpha_5$	$\alpha_6$	$\alpha_7$
$U_{dAV}/U_{dAV0}$								
$I_{dAV}/I_{dAV0}$								
<b>Form factor</b>								
<b>Ripple factor</b>								

Draw the transfer characteristic  $U_{dAV}/U_{dAV0} = f(\alpha)$ .

Compare the measurements with the expected theoretical values.

#### 4) Recording on the oscilloscope (Use $\alpha = 90^\circ$ )

##### **Note**

*Since the basic instrument set does not normally allow simultaneous measurements, the measures may have to be carried out successively.*

4.1) Recording the supply  $U_v$  and load  $U_d$  voltages.

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 (voltage  $U_v$ )

Channel 2 (voltage  $U_d$ )

4.2) Recording the voltage  $U_v$  and the load current  $I_d$ .

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

Channel 1 ( $U_v$  voltage)


Channel 2 (current  $I_d$ , proportional to voltage across shunt resistor  $R_s = 1 \Omega$ ): 1 V/div.

# SINGLE-PULSE CONVERTER OHMIC-INDUCTIVE LOAD AND FREEWHEELING DIODE

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

Circuit diagram

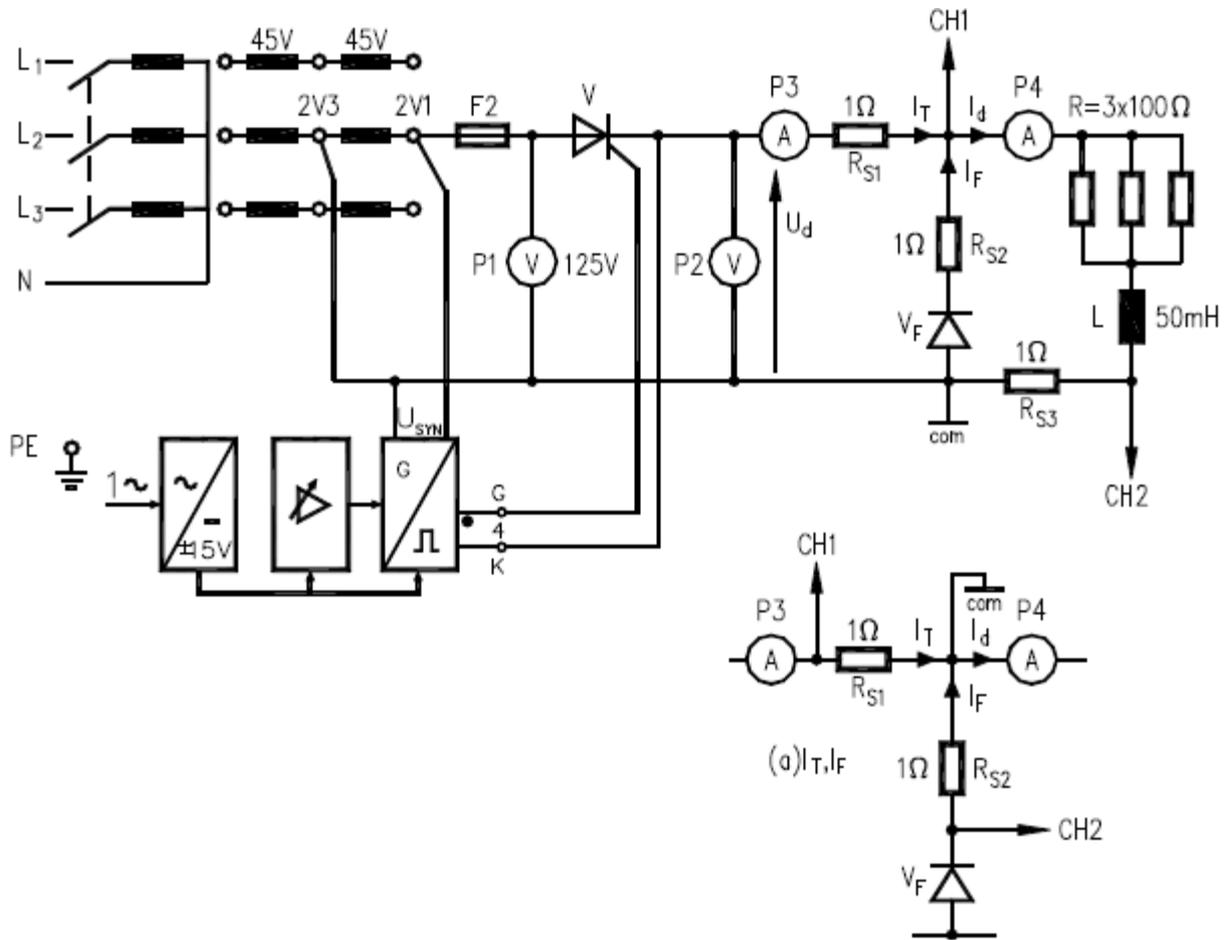

## Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding detail (a) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V1/2V3 of the transformer.

Connect the pulse transformer 4 to gate/cathode circuit of the SCR: socket marked with a dot to the gate.

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 10 V.

#### 2.2) Control unit DL2616

Control angle  $\alpha_o$  switch on  $0^\circ$  position.

“Pulse shape” switch on pulse train position.

Inhibit voltage  $U_{INH} = 15$  V (open).

### 3) Supply the circuit and measure:

3.1) the rms value  $U_v$  of the supply voltage by the voltmeter P1;

3.2) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the output voltage by the voltmeter P2;

3.3) the average value  $I_{TAV}$  and the rms value  $I_{TRMS}$  of the SCR current by the ammeter P3.

3.4) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the direct current by the ammeter P4.

Enter the measured value as a function of the gate angle  $\alpha$  in the table below.

$U_v =$

$\alpha$ (°)	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$	$\alpha_5$	$\alpha_6$	$\alpha_7$
$U_{dAV}$ (V)								
$U_{dRMS}$ (V)								
$I_{dAV}$ (A)								
$I_{dRMS}$ (A)								
$I_{TAV}$ (A)								
$I_{TRMS}$ (A)								

$\alpha$ (°)	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$	$\alpha_5$	$\alpha_6$	$\alpha_7$
$U_{dAV}/U_{dAV0}$								
$I_{dAV}/I_{dAV0}$								
<b>Form factor</b>								
<b>Ripple factor</b>								

Draw the transfer characteristic  $U_{dAV}/U_{dAV0} = f(\alpha)$ .

Compare measurements with the expected theoretical values.

### 4) Recording on the oscilloscope (use $\alpha = 90^\circ$ )

**Note:** Since the basic instrument set does not normally allow simultaneous measurements, the measures may have to be carried out successively.

4.1) Recording the load voltage  $U_d$  and the load current  $I_d$ .

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 (voltage  $U_v$ )

Channel 2 (current  $I_d$  proportional to voltage at shunt  $R_{S3} = 1 \Omega$ ): 1 V/div.

4.2) Recording the SCR current  $I_T$  and the free-wheeling diode current  $I_F$

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

Channel 1 (current  $I_T$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 500 mV/div.

Channel 2 (current  $I_F$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 500 mV/div.

## EXPERIMENT THREE

### TWO-PULSE CONVERTERS

#### (A) TWO-PULSE MIDPOINT CONVERTER (BI-PHASE)

##### INTRODUCTION

Midpoint converters must include a transformer with centre tapped winding on the secondary side to have two partial and equal ac voltages and two SCRs, as shown in Fig. 1.

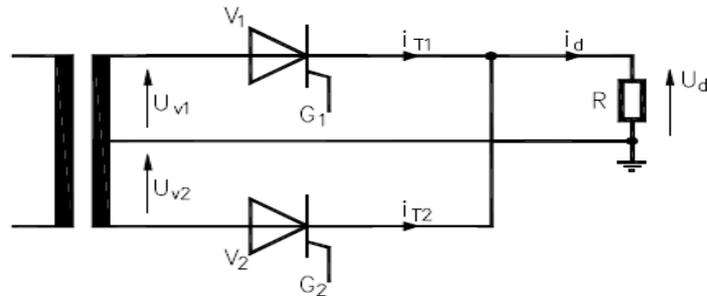


Fig.1 Two-pulse converter, with ohmic load

If we refer the voltages  $U_{v1}$  and  $U_{v2}$  to the midpoint (neutral) these voltages are in phase opposition and for positive anode voltages the SCRs are alternatively fired and conduct the current of the corresponding line voltage from firing point to the zero cross-over.

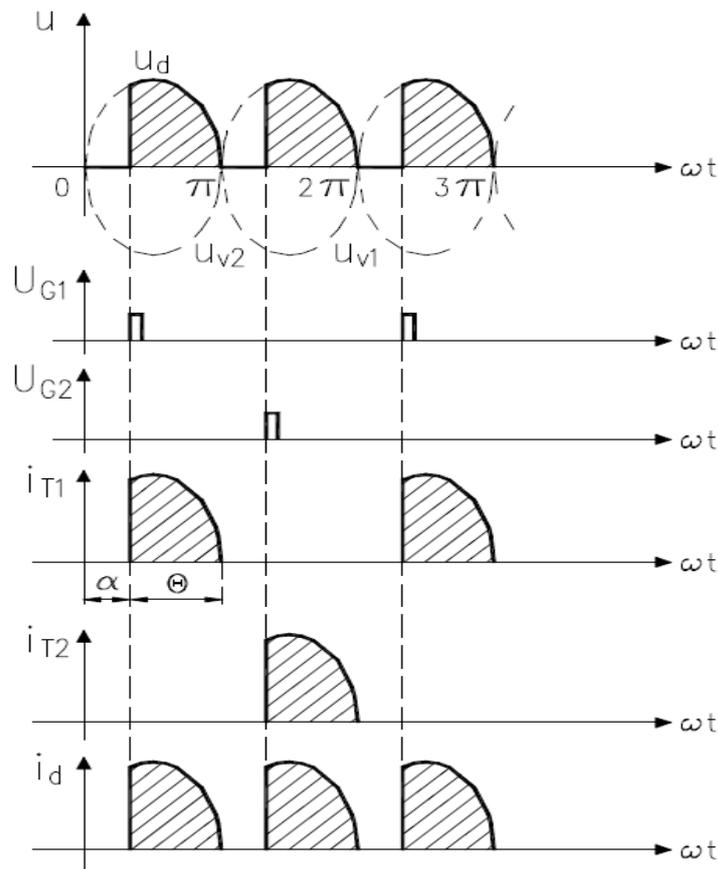


Fig.2 Voltage and current time profiles

The load current  $i_d$  is composed of the two SCR currents; it is an intermittent (discontinuous) pulsating current. The average value of output voltage is

$$U_{dAV} = 0.5 U_{dAV0} (1 + \cos \alpha)$$

Where

$$U_{dAV0} = 0.9 U_{v1} = 0.9 U_{v2}$$

is the average value for the gate angle  $\alpha = 0^\circ$

**Ohmic-inductive load**

Circuits containing R and L in series are a load type frequently found in practice.

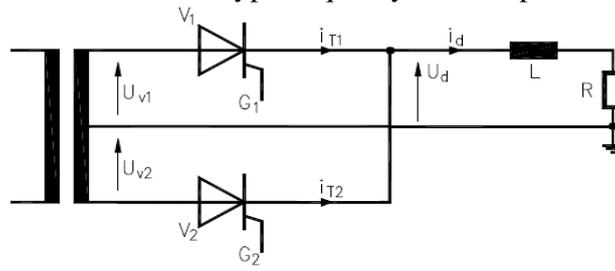


Fig.3 Converter with ohmic-inductive load

The inductance prevents any abrupt load current changes. To understand how the circuit operates, initially assume that the load phase angle  $\phi = \arctan \omega L/R$  is adjusted for a non-intermittent operation (very large smoothing choke L), as shown in Fig.4.

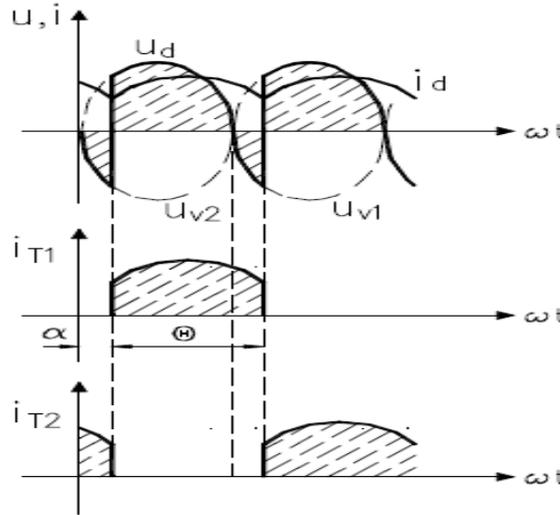


Fig.4 Voltage and current time profiles, RL load, non-intermittent (continuous) operation

At the control angle  $\alpha$  the direct current is alternatively conducted through the SCRs  $V_1$  and  $V_2$  that conduct current through the zero crossing of supply voltages until the following SCR is triggered. The conduction angle is  $\Theta = 180^\circ$ . The dc voltage takes on +ve and -ve values.

The output voltage average value is positive in control range  $0^\circ \leq \alpha < 90^\circ$  (energy is supplied to load from the mains), it is zero at  $\alpha = 90^\circ$  and negative for  $\alpha > 90^\circ$  (energy is transferred from the load back into the mains; this type of operation can only continuously be carried out if there is an energy source present in the load).

The average value of output voltage with non-intermittent (continuous) operation is

$$U_{dAV} = (2U_{vM1}/\pi) \cos\alpha = (2U_{vM2}/\pi) \cos\alpha$$

With increasing the control angle  $\alpha$  the operation becomes intermittent after a limit control angle has been exceeded, as shown in Fig. 5. To find the average output voltage the conduction angle  $\theta$  should be determined.

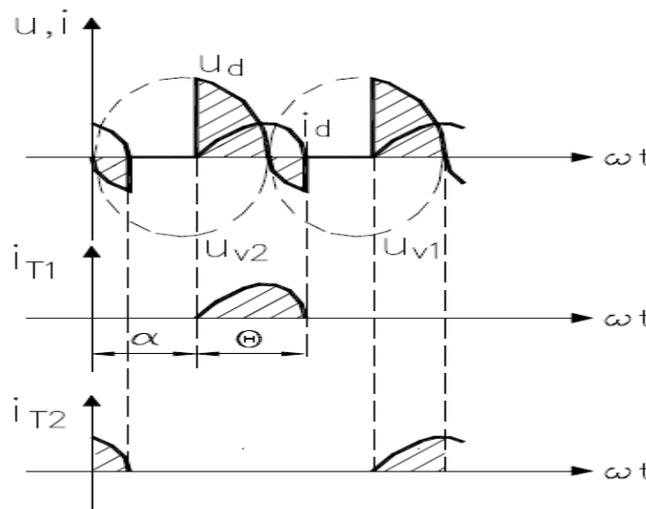


Fig.5 Voltage and current time profiles, RL load, intermittent (discontinuous) operation

## (B) SINGLE-PHASE BRIDGE CONVERTERS

These converters can be half-controlled, as shown in Figs. 6 (a) and (b) or fully-controlled as in Fig. 6(c).

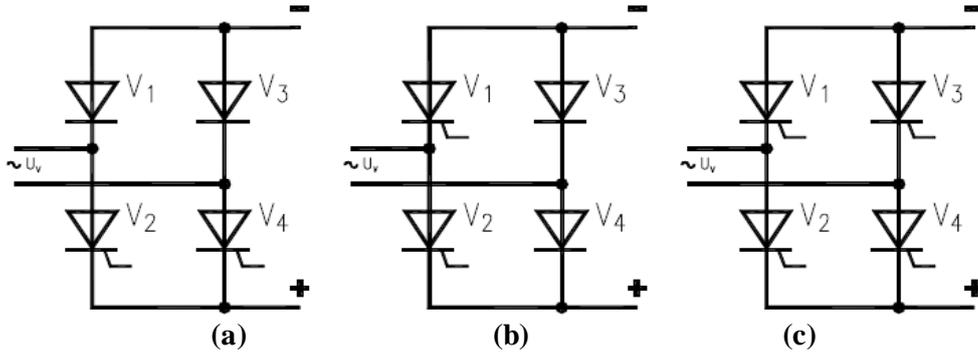


Fig.6 (a) and (b) are half-controlled bridges while (c) is a fully-controlled bridge

### Ohmic load

With ohmic load the operation of the three bridges is similar and the load current voltages are shown in Fig. 7

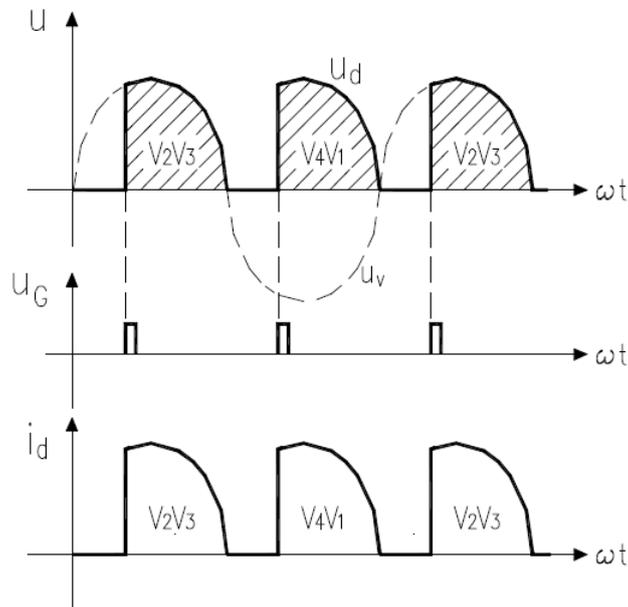


Fig. 7 Time profiles of converters (a), (b) and (c), ohmic load

Current time profile is intermittent (discontinuous) as the extinction angle coincides with the end of the half cycle. At the control angle  $\alpha = 0^\circ$  the dc voltage is maximum and the average values is

$$U_{dAV0} = 0.9 U_v$$

## Fully-controlled bridge, ohmic-inductive load

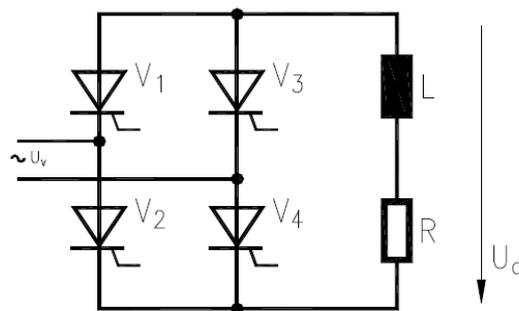


Fig. 8 Fully-controlled bridge converter with ohmic-inductive load

When the trigger pulse is applied to two SCR gates at the same time, each pair of the series connected SCRs in the bridge diagonals ( $V_2$ - $V_3$  or  $V_4$ - $V_1$ ) conducts alternatively, as shown in the following figure for different control angles.

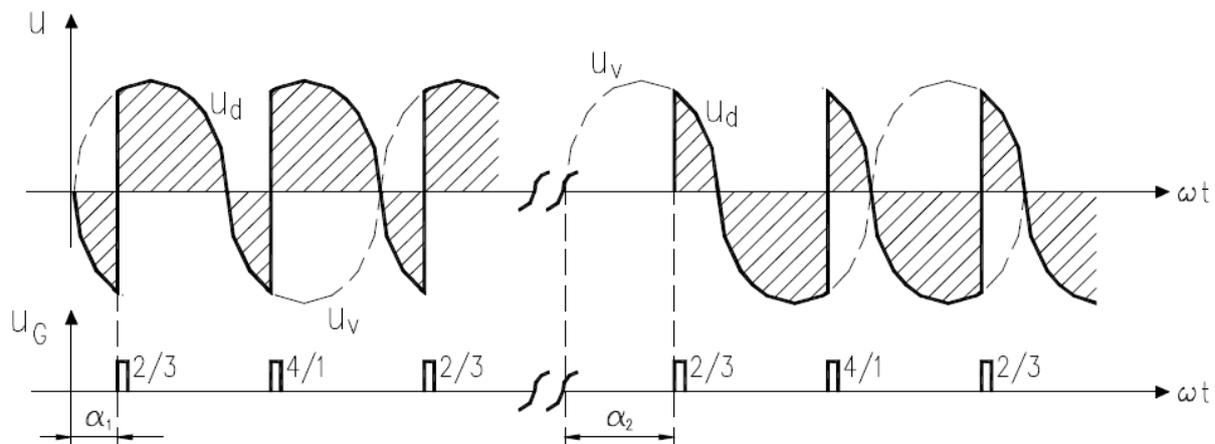


Fig. 9 Voltage time profile, fully-controlled bridge converter with ohmic-inductive load, non-intermittent (continuous) operation

For all control angles  $\alpha > 0^\circ$  the time profile of output voltage has positive and negative instantaneous values and its average value is positive in the control range  $0^\circ < \alpha < 90^\circ$  and negative in the range  $90^\circ < \alpha < 180^\circ$  (regenerative operation).

Each time an SCR pair is triggered, a commutating process begins: during the commutation duration all four SCRs conduct and in this brief overlap duration a short circuit of the supply transformer results and the direct voltage is zero.

Neglecting overlap and other circuit losses, the average value of output voltage with continuous operation is

$$U_{dAV} = (2U_{vM}/\pi) \cos\alpha$$

With increasing the control angle  $\alpha$  the operation becomes intermittent (discontinuous) after a limit control angle has been exceeded. To find the average output voltage the conduction angle  $\theta$  should be first determined.

**Note:** Read the theoretical part of experiment 2.

## Half-controlled bridge, ohmic-inductive load (Topology 1)

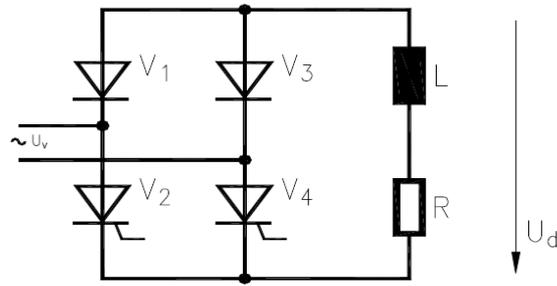


Fig. 10 Half-controlled converter with ohmic-inductive load

After the gate-controlled turn-on time (control angle  $\alpha$ ), the SCR  $V_2$  and the diode  $V_3$  conduct until the supply ac voltage crosses the zero. Afterwards there is a voltage across the diode  $V_1$  in the forward direction and the diode  $V_1$  conducts and the load current commutates from diode  $V_3$  to diode  $V_1$ : the magnetic energy stored in the inductance  $L$  maintains the current through the path SCR  $V_2$  and diode  $V_1$  until the coil has been discharged through the resistance  $R$ . Fig. 11 shows the non-intermittent (continuous) operation.

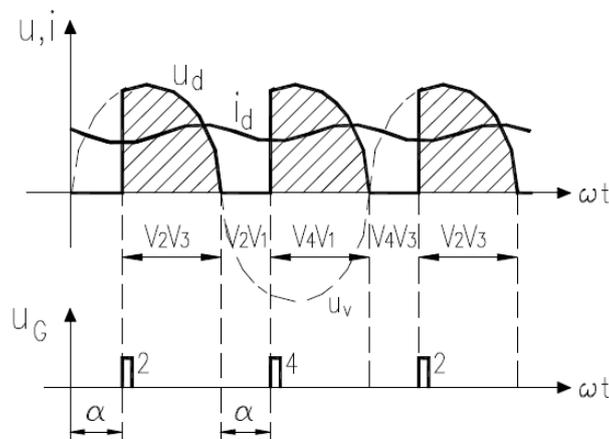


Fig. 11 Voltage and current profiles, half-controlled converter with ohmic-inductive load, non-intermittent (continuous) operation

Until the following SCR  $V_4$  is triggered, the load circuit is short-circuited via the paired arm  $V_2/V_1$  (free-wheeling) until the following SCR  $V_4$  is turned on while the dc voltage is zero and the feedback into ac supply is not possible.

SCRs and diodes conduct over  $180^\circ$  independently of the control angle, while the dc voltage can not be controlled to zero and the upper control limit is approximately  $150^\circ$ .

At large control angles ( $\alpha > 90^\circ$ ) the free-wheeling current can pass through zero before the following SCR is turned on: in that case the operation is intermittent (discontinuous), as shown in Fig. 12

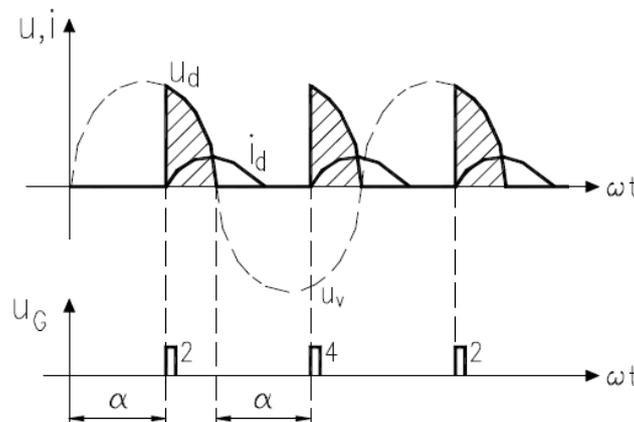


Fig. 12 Voltage and current profiles, half-controlled converter with ohmic-inductive load, intermittent operation

### Half-controlled bridge, ohmic-inductive load (Topology 2)

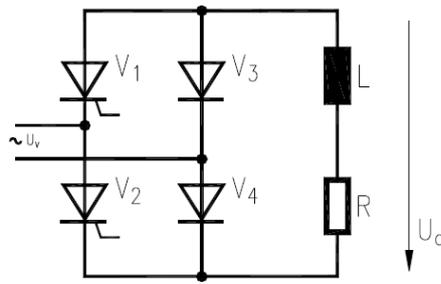


Fig. 13 Half-controlled converter with ohmic-inductive load

After the gate-controlled turn-on time (control angle  $\alpha$ ), the SCR  $V_2$  and the diode  $V_3$  conduct until the supply ac voltage crosses the zero. Afterwards there is a voltage across the diode  $V_4$  in the forward direction and so the diodes  $V_4$  and  $V_3$  form a direct free-wheeling arm and prevent a delivery of the energy back into the mains. The time profile of direct voltage is identical with the time profile of case (a), as shown

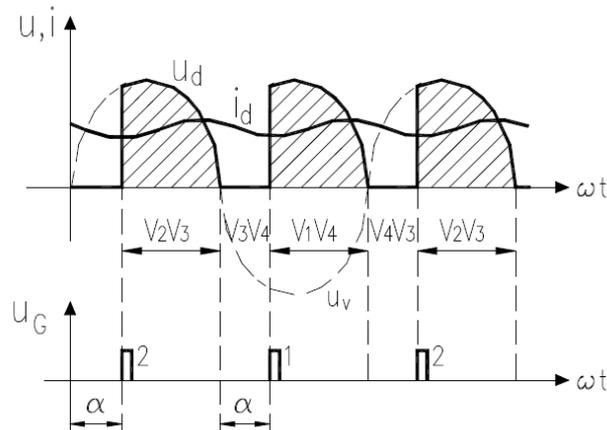


Fig. 14 Voltage and current profiles, half-controlled converter with ohmic-inductive load, non-intermittent operation

When the control angle  $\alpha > 0^\circ$  the conduction angle of diodes  $V_3$  and  $V_4$  is higher than that one of the SCRs  $V_2$  and  $V_1$  and so the diodes are loaded more. The control angle can be changed from  $0^\circ$  to  $180^\circ$  and therefore the direct voltage can be controlled down to zero.

Neglecting circuit losses, the average value of the output voltage for the two topologies of half controlled bridge rectifiers can be expressed as


$$U_{dAV} = (U_{vM}/\pi)(1 + \cos \alpha)$$

## TWO-PULSE MIDPOINT CONVERTER OHMIC-INDUCTIVE LOAD

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

Circuit diagram

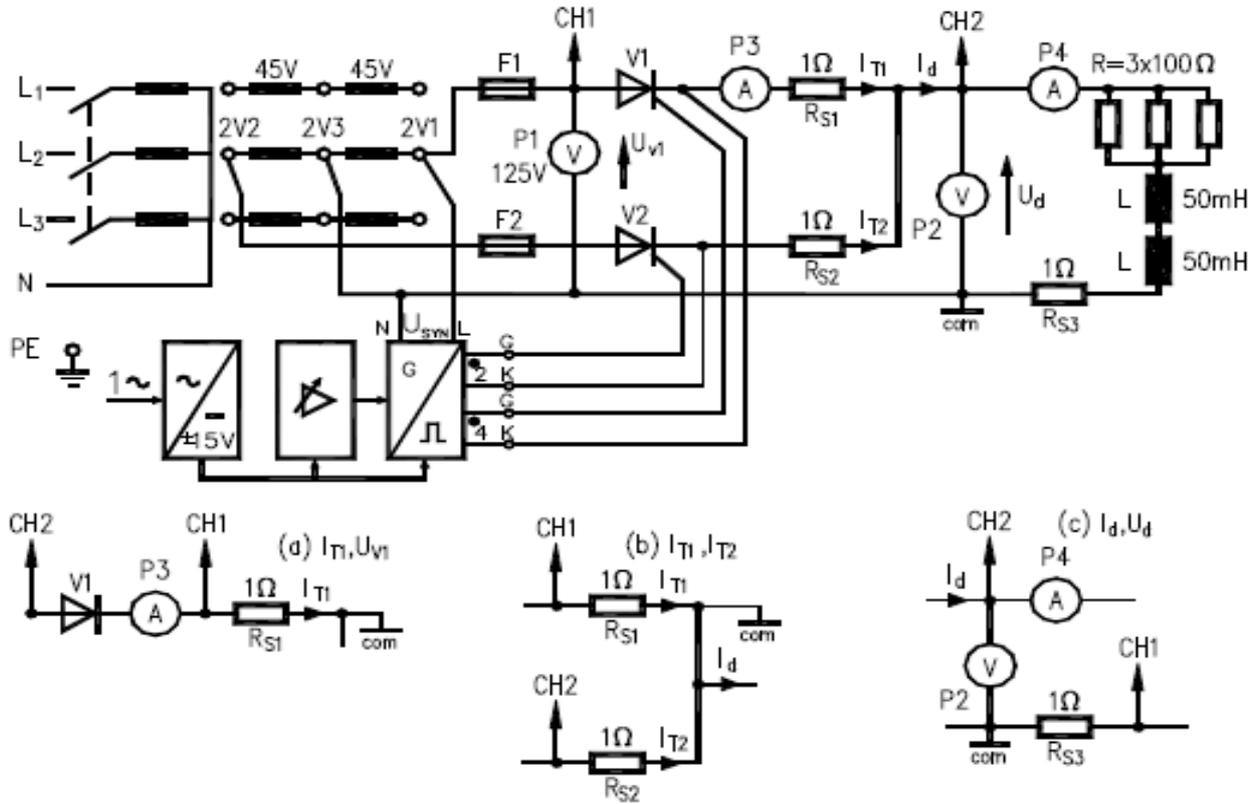

## Experiment procedure

Assemble the circuit according with the foregoing circuit diagram, disregarding details (a), (b) and (c) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V1/2V3 of the transformer.

Connect pulse transformers 2 & 4 to gate/cathode circuit of SCRs  $V_2$  &  $V_1$ : socket marked with a dot to the gate

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 10 V.

#### 2.2) Control unit DL2616

Control angle  $\alpha_0$  switch on  $0^\circ$  position.

“Pulse shape” switch on pulse train position.

Inhibit voltage  $U_{INH} = 15$  V (open).

### 3) Supply the circuit and measure:

3.1) the rms value  $U_{v1}$  of the supply voltage by the voltmeter P1;

3.2) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the output voltage by the voltmeter P2;

3.3) the average value  $I_{T1AV}$  and the rms value  $I_{T1RMS}$  of the SCR  $V_1$  current by the ammeter P3;

3.4) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the output current by the ammeter P4.

Enter the measured value as a function of gate angle  $\alpha$  in the table below.

$U_{v1} =$

$\alpha$ ( $^\circ$ )	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$
$U_{dAV}$ (V)					
$U_{dRMS}$ (V)					
$I_{dAV}$ (A)					
$I_{dRMS}$ (A)					
$I_{T1AV}$ (A)					
$I_{T1RMS}$ (A)					

Evaluate the various characteristic data of the converter and compare these with the theoretical values.

Draw the transfer characteristic  $U_{dAV}/U_{dAV0} = f(\alpha)$ .

### 4) Recording on the oscilloscope (Use $\alpha = 60^\circ$ )

4.1) Recording the supply  $U_{v1}$  and output  $U_d$  voltages.

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 (voltage  $U_{v1}$ ) and Channel 2 (voltage  $U_d$ )

4.2) Recording the current  $I_{T1}$  and the voltage  $U_{v1}$  at SCR  $V_1$

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

Channel 1 (current  $I_{T1}$  proportional to voltage at shunt  $R_{S1} = 1\Omega$ ): 500 mV/div.

Channel 2 ( $U_{v1}$  voltage)

4.3) Recording the diode currents  $I_{T1}$  and  $I_{T2}$

Oscilloscope setting

Assemble the measuring circuit according with detail (b).

Channel 1 (current  $I_{T1}$  proportional to voltage at shunt  $R_{S1} = 1\Omega$ ): 1 V/div.

Channel 2 (current  $I_{T2}$  proportional to voltage at shunt  $R_{S2} = 1\Omega$ ): 1 V/div.

4.4) Recording the current  $I_d$  and the voltage  $U_d$ .

Oscilloscope setting

Assemble the measuring circuit according with detail (c).


Channel 1 (current  $I_d$  proportional to voltage at shunt  $R_{S3} = 1\Omega$ ): 1 V/div.

Channel 2 ( $U_d$  voltage)
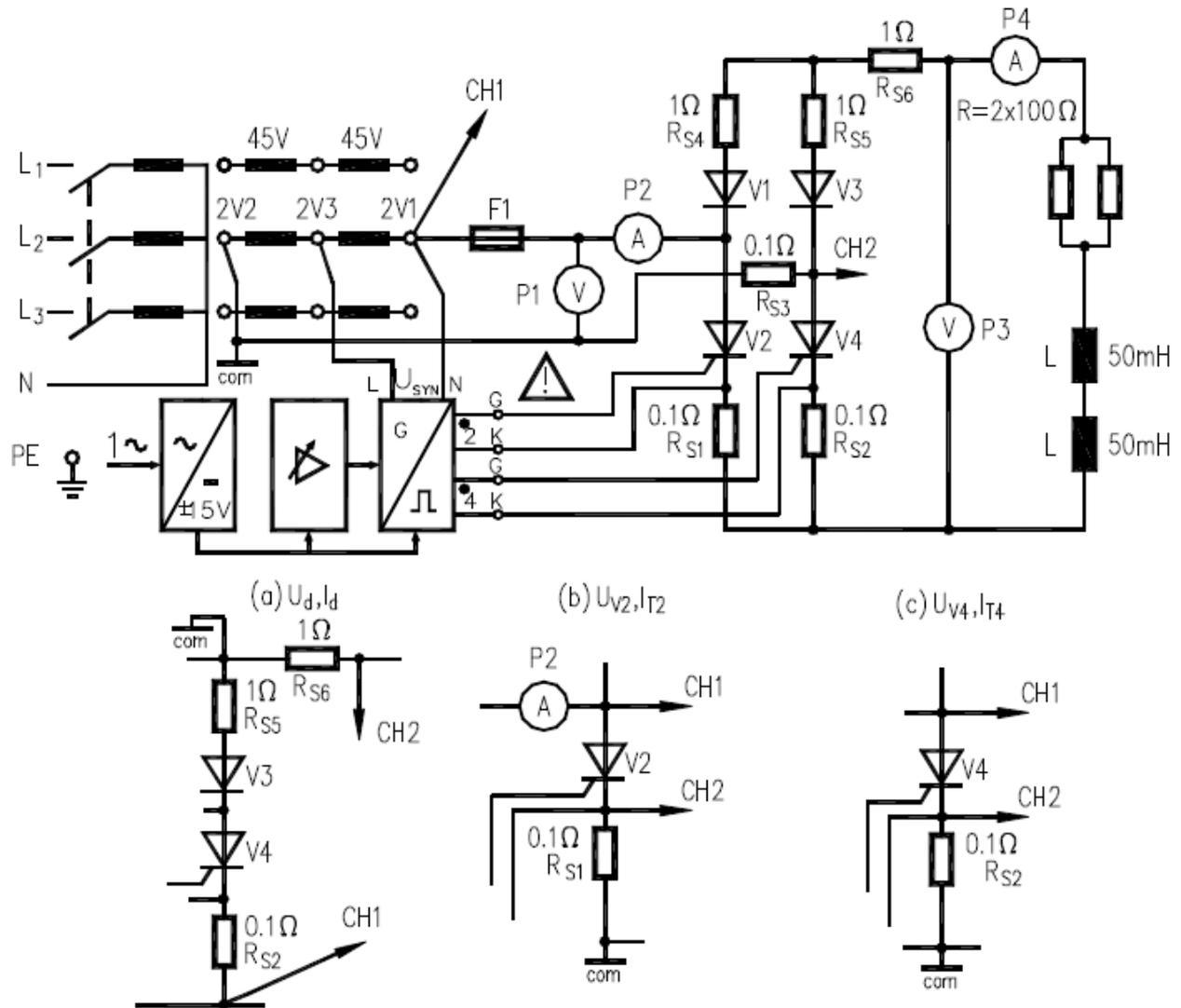
## HALF-CONTROLLED BRIDGE, OHMIC-INDUCTIVE LOAD (TOPOLOGY 1)

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data



## Experiment procedure

Assemble the circuit according to the foregoing circuit diagram, disregarding details (a), (b) and (c) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V3/2V1 of the transformer.

Connect pulse transformers 2 & 4 to gate/cathode circuit of SCRs  $V_2$  &  $V_4$ : socket marked with a dot to the gate

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 10 V.

#### 2.2) Control unit DL2616

Control angle  $\alpha_o$  switch on  $0^\circ$  position.

“Pulse shape” switch on pulse train position.

Inhibit voltage  $UINH = 15$  V (open).

### 3) Supply the circuit and measure:

3.1) the rms value  $U_v$  of the supply voltage by the voltmeter P1;

3.2) the rms value  $I_v$  of the supply current by the ammeter P2;

3.3) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the output voltage by the voltmeter P3;

3.4) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the output current by the ammeter P4.

Enter in the table the measured value as a function of gate angle  $\alpha$ .

$\alpha$ ( $^\circ$ )	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$
$U_v$ (V)					
$I_v$ (A)					
$U_{dAV}$ (V)					
$U_{dRMS}$ (V)					
$I_{dAV}$ (A)					
$I_{dRMS}$ (A)					

Compare measurements with the expected theoretical values.

### 4) Recording on the oscilloscope (Use $\alpha = 60^\circ$ )

4.1) Recording the supply voltage  $U_v$  and current  $I_v$ .

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 (voltage  $U_v$ )

Channel 2 (current  $I_v$  proportional to voltage at shunt  $R_{S3} = 0.1 \Omega$ )

4.2) Recording the voltage  $U_d$  and current  $I_d$ . Oscilloscope setting.

Assemble the measuring circuit according with detail (a).

Channel 1 ( $U_d$  voltage)

Channel 2 (current  $I_d$  proportional to voltage at shunt  $R_{S6} = 1 \Omega$ )

4.3) Recording the SCR  $V_2$  voltage and current

Oscilloscope setting:

Assemble the measuring circuit according with detail (b).

Channel 1 (voltage  $U_{v2}$ )

Channel 2 (current  $I_{T2}$  proportional to voltage at shunt  $R_{S1} = 0.1 \Omega$ )

4.4) Recording the SCR  $V_4$  voltage and current

Oscilloscope setting:

Assemble the measuring circuit according with detail (c).

Channel 1 (voltage  $U_{v4}$ )

Channel 2 (current  $I_{T4}$  proportional to voltage at shunt  $R_{S2} = 0.1 \Omega$ )

## EXPERIMENT FOUR

### THREE-PHASE BRIDGE CONVERTERS

#### INTRODUCTION

The three-phase fully-controlled bridge circuit is shown below

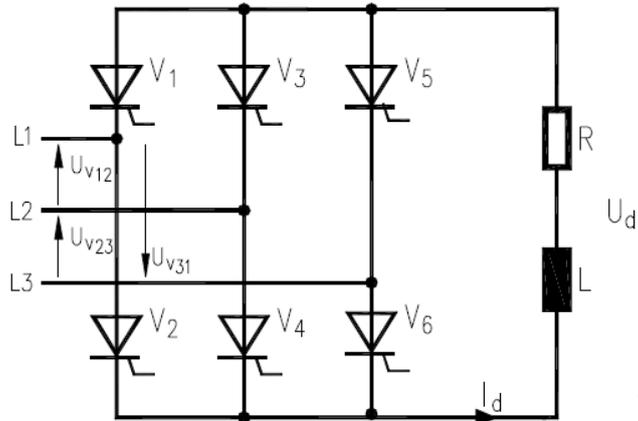


Fig. 1 Three-phase fully-controlled bridge converter with ohmic-inductive load

Two SCRs always conduct simultaneously and the trigger pulses have to be applied simultaneously to the two concerned SCRs, that in this way need double pulses: this means that each SCR requires two pulses (main and secondary pulse) which are phase shifted by  $60^\circ$  with respect to each other and that the secondary pulse must be synchronous with the trigger pulse of the following SCR.

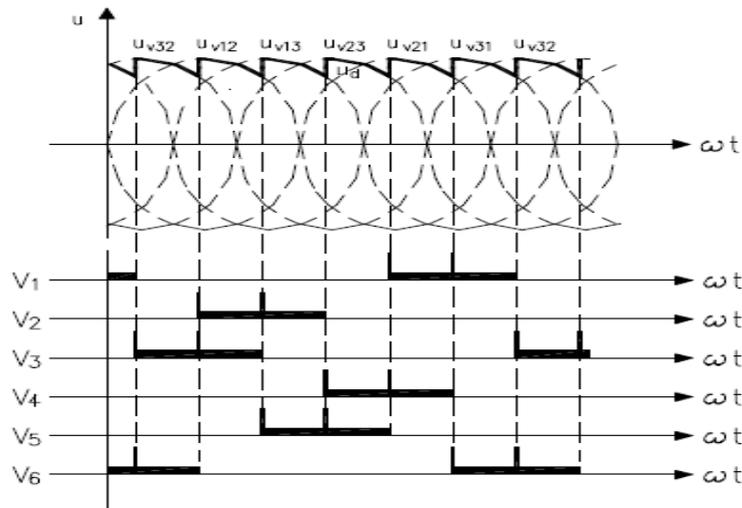


Fig. 2 Voltage time profile, 3-phase fully-controlled bridge converter with ohmic-inductive load

With ohmic load the conduction is not-intermittent for control angle up to  $60^\circ$  and becomes intermittent for control angles  $60^\circ < \alpha < 120^\circ$ : finally the direct voltage is zero for  $\alpha > 120^\circ$ .

The average output voltage is

$$U_{dAV} = 1.35 U_{v12}$$

For an ohmic-inductive load the direct current is smoothed by the energy stored in the choke until intermittent operation occurs at limit control angle.

Beyond the control angle  $60^\circ$  the direct voltage has negative areas and the operation is said to be regenerative.

For continuous (non-intermittent) operation the average output voltage can be expressed as

$$U_{dAV} = (1.35 U_{v12}) \cos \alpha$$


**Note:** Read the theoretical part of experiments 2 and 3.

## THREE-PHASE FULLY-CONTROLLED BRIDGE, OHMIC-INDUCTIVE LOAD

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

Circuit diagram

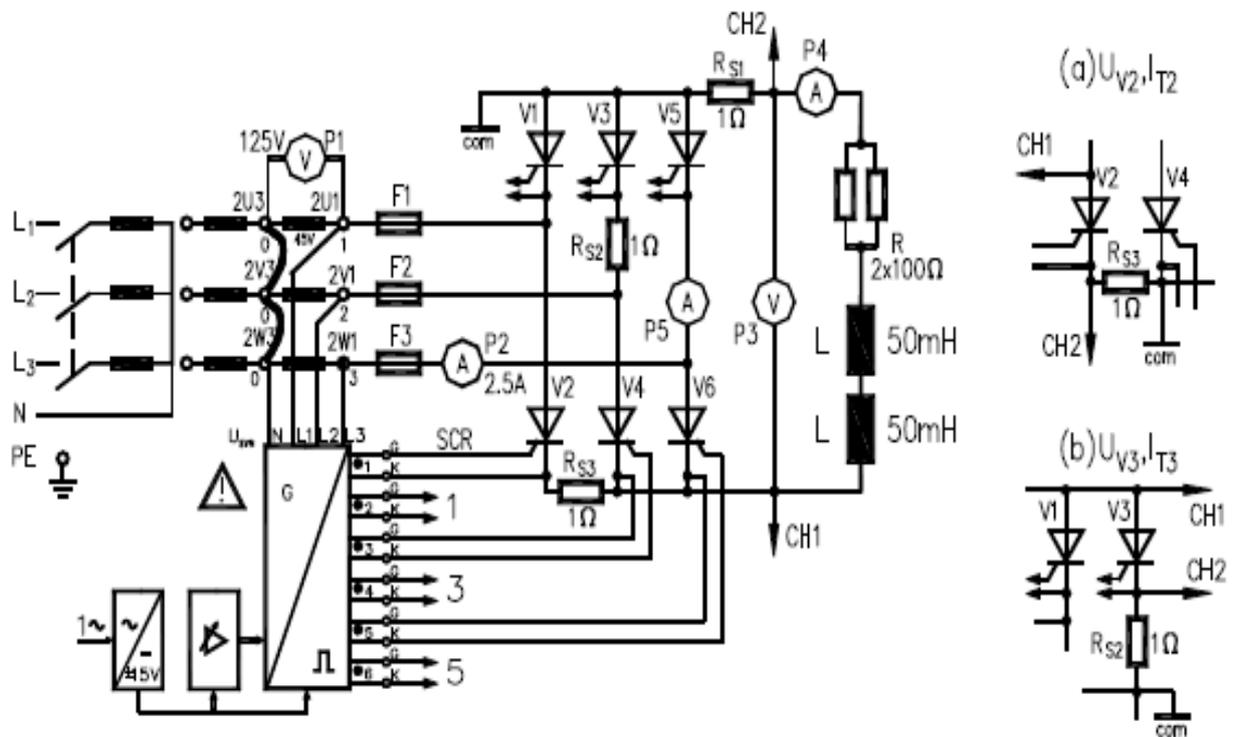

## Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding details (a) and (b) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2617 to power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect terminals  $L_1/L_2/L_3/N(U_{SYN})$  of control unit to transformer terminals 2U1/2V1/2W1/2U3 respectively.

Connect the pulse transformers 1, 2, 3, 4, 5 and 6 to gate/cathode circuit of the SCRs  $V_2, V_1, V_4, V_3, V_6$  and  $V_5$ : socket marked with a dot to the gate.

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 10 V.

#### 2.2) Control unit DL2617

Analog control switch on “∩” position

Control angle  $\alpha_o$  switch on 30° position.

“Pulse shape” switch on single pulse position.

Select MAIN + SEC PULSE

Inhibit voltage  $UINH = 15$  V (open).

#### 2.3) Natural commutating point

In order to use the practically control the converter must set with the control angle

$\alpha=0^\circ$  at the natural commutating point with the reference voltage  $U_o = 10$  V.

Set  $\alpha_o = 30^\circ$  and  $U_c = 10$  V.

Supply the circuit and check the correct phase sequence (green led lights).

If the oscilloscope displays a six-pulse rectified voltage the control angle is  $\alpha = 0^\circ$ .

### 3) Voltage and current measurements

Supply the circuit and measure:

3.1) the rms value  $U_{v3}$  of the phase voltage by the voltmeter P1;

3.2) the rms value  $I_{v3}$  of the line current by the ammeter P2;

3.3) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the output voltage by the voltmeter P3;

3.4) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the output current by the ammeter P4.

3.5) the average value  $I_{T5AV}$  and the rms value  $I_{T5RMS}$  of the SCR  $V_5$  current by the ammeter P5.

Enter the measured value as a function of the gate angle  $\alpha$  in the following table.

$\alpha$ (°)	0	$\alpha_1$	$\alpha_2$	$\alpha_3$	$\alpha_4$
$U_{v3}$ (V)					
$I_{v3}$ (A)					
$U_{dAV}$ (V)					
$U_{dRMS}$ (V)					
$I_{dAV}$ (A)					
$I_{dRMS}$ (A)					
$I_{T5AV}$ (A)					
$I_{T5RMS}$ (A)					

Draw the transfer characteristic  $U_{dAV}/U_{dAV0} = f(\alpha)$ . Compare measurements with expected theoretical values.

### 4) Recording on the oscilloscope (Use $\alpha = 60^\circ$ )

4.1) Recording the output voltage  $U_d$  and current  $I_d$

Oscilloscope setting: DC coupling; Yt mode. Trigger: AC Line.

Channel 1 ( $U_d$  voltage); Channel 2 (current  $I_d$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 1 V/div.

4.2) Recording the voltage  $U_{V2}$  and the current  $I_{T2}$  at SCR  $V_2$

Oscilloscope setting: Assemble the measuring circuit according with detail (a).

Channel 1 ( $U_{V2}$  voltage); Channel 2 (current  $I_{T2}$  proportional to voltage at shunt  $R_{S3} = 1 \Omega$ ): 1 V/div.

4.3) Recording the voltage  $U_{V3}$  and the current  $I_{T3}$  at SCR  $V_3$

Oscilloscope setting: Assemble the measuring circuit according with detail (b).

Channel 1 ( $U_{V3}$  voltage); Channel 2 (current  $I_{T3}$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 1 V/div.

## EXPERIMENT FIVE

### STEP-DOWN (BUCK) CONVERTER

#### INTRODUCTION

As the name implies, this converter produces a lower average output voltage than the dc input voltage. Its main application is in regulated dc power supplies and dc motor speed control.

The basic circuit is shown in Fig.1, where pulse-width modulation (PWM) control is presumed.

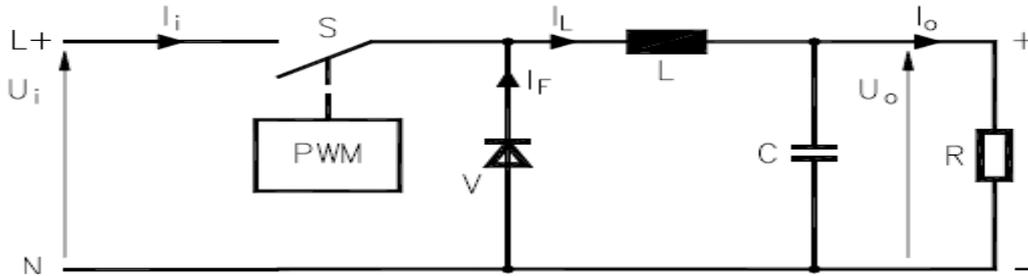


Fig. 1 Step-down (buck) converter

The controllable switch S supplies the LC low-pass filter with a voltage  $U_i$  while the fast diode V allows the free-wheeling flow of the current during the blocking phase of the switch.

The typical voltage and current characteristics are shown in Fig.2.

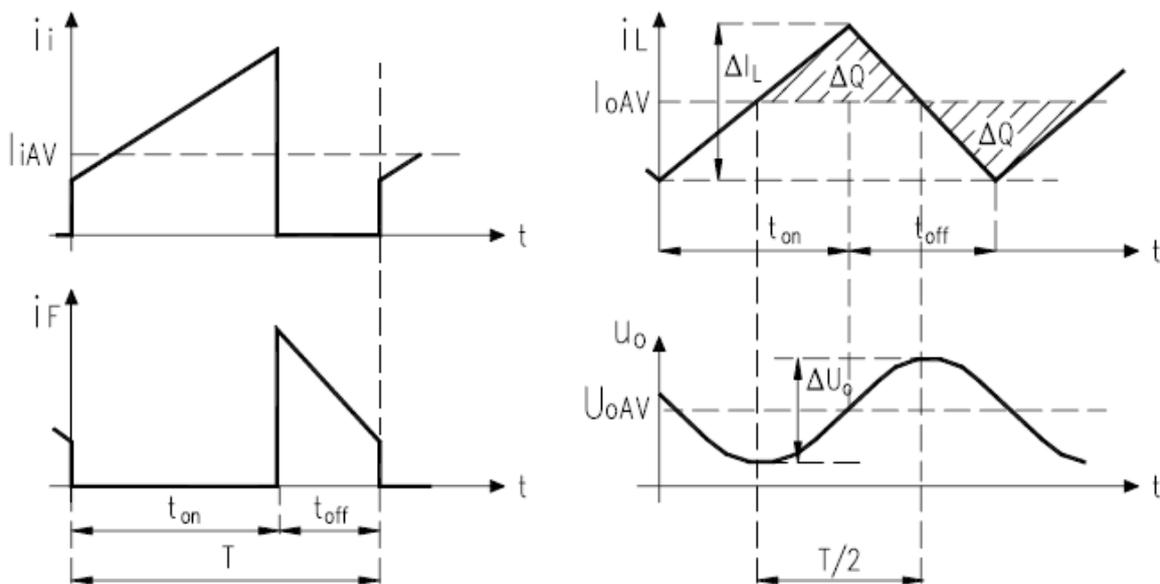


Fig. 2 Voltage and current characteristics, step-down converter

During the interval when the switch S is on, the diode becomes reverse biased and the input provides energy to the load R as well as to the inductor L.

The voltage across the inductor L is  $U_i - U_{oAV}$  and causes a linear increase in the inductor current  $I_L$  equal to:

$$(\Delta I_L)_{\text{rising}} = (U_i - U_{oAV}) t_{\text{on}} / L$$

During the interval when the switch S is off, the inductor current flows through the diode, transferring some of its stored energy to the load R. The voltage across the inductor is  $-U_{oAV}$  now and causes a linear decrease of the inductor current  $I_L$  equal to:

$$(\Delta I_L)_{\text{falling}} = U_{oAV} t_{\text{off}} / L$$

Since in the steady-state operation the variations of the current  $I_L$  must be equal this implies that:

$$U_{oAV} = U_i t_{\text{on}} / T = U_i D$$

The average value  $I_{oAV}$  of the current flowing through the load R is equal to the average value  $I_{LAV}$  of the inductor current. From Fig.2 we observe that

$$I_{iAV}T = I_{LAV}t_{on}$$

So

$$I_{oAV} = I_{LAV} = I_{iAV}T/t_{on} = I_{iAV}/D$$

The peak-to-peak ripple in the output voltage can be calculated by considering the waveforms shown in Fig.2 for a continuous conduction mode of operation. Assuming that all the ripple component of the inductor current  $I_L$  flows through the capacitor C and its average value flows through the load R, since the shaded area represents the additional charge  $\Delta Q$ , it results

$$\Delta U_o = \Delta Q/C = (\Delta I_L T)/(8C)$$

During  $t_{off}$  interval it results

$$\Delta I_L = (U_{oAV})(t_{off}/L) = U_{oAV}(1-D)T/L$$

Therefore, replacing into the previous equation, we have

$$\Delta U_o = U_{oAV}(1-D)/(8f^2LC)$$

Where  $f = 1/T$  is the switching frequency

### Remark

The conduction mode of the converter can be continuous or discontinuous, based on the inductor current value. Being at the boundary between the continuous and the discontinuous mode, by definition, the inductor current goes to zero at the end of the  $t_{off}$  interval.

At this boundary (subscript B), the average inductor current is:

$$I_{LBAV} = \Delta I_L/2 = (U_i - U_{oAV})D/(2fL) = I_{oBAV}$$

and so, if during an operating condition it results  $I_{oAV} < I_{LBAV}$  then the operation will become discontinuous.



## Experiment procedure

Assemble the circuit according to the foregoing circuit diagram, disregarding detail (a) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and PWM control unit DL2619 to power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the pulse output  $S_1$  to gate/source circuit of the MOSFET  $V_1$ : socket marked with a dot to the gate.

### 2) Preliminary calculations

#### 2.1) Input voltage of the converter

Star connected transformer:  $U_{v_0} = 2 \times 45 = 90 \text{ V}$ .

Rectified voltage and dc input voltage of the converter:

$$U_{dAV} = U_{iAV} = 2.342 U_{v_0} = 2.342 \times 90 \cong 210.8 \text{ V}$$

#### 2.2) Input current of the converter

The current on every line supplying the bridge flows for  $2/3$  of the period and so, being the permissible current  $I_v = 1.5 \text{ A}$  on the secondary phase winding of the mains transformer, the permissible rectified current is  $(3/2)^{0.5} \times 1.5 = 1.224 \times 1.5 = 1.84 \text{ A}$  but, as a precaution, the permissible input current is assumed equal to  $1.5 \text{ A}$

#### 2.3) Output voltage of the converter

When the switching frequency is  $f = 4000 \text{ Hz}$  and the control voltage  $U_c = 3.5 \text{ V}$  approx, the duty ratio is 50%

The output voltage of the converter is  $U_{oAV} = U_{iAV} D = 210.8 \times 0.5 = 105.4 \text{ V}$

#### 2.4) Output current of the converter

The permissible output current of the converter depends on the permissible currents for the used components.  
MOSFET:  $10 \text{ A}$ .

Load inductance:  $2.5 \text{ A}$ .

Load resistance  $100 \Omega$ :  $1 \text{ A}$ .

The input current of the converter is smaller than the output current in accordance with the duty ratio and so, if a load resistance  $100 \Omega$  is assumed the output current is  $105.4/100 = 1.05 \text{ A}$

### 3) Basic settings

#### 3.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/ $\pm$ 10V) switch on (0/+10V) position.

Set point potentiometer to  $3.5 \text{ V}$ .

#### 3.2) Control unit DL2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 4000 \text{ Hz}$ : coarse adjustment "x100" and fine adjustment "40".

Inhibit voltage  $U_{INH} = 15 \text{ V}$  (open).

#### 3.3) Meters

Set AV/AC+DC measurements for voltmeters P1/P3 and ammeters P2/P4.

Voltmeters P1/P3: measuring range  $300 \text{ V}$ .

Ammeters P2/P4: measuring range  $3 \text{ A}$  ( $1 \text{ A}$ ).

#### 3.4) MOSFET

Connect the RCD suppressor circuit.

#### 3.5) Free-wheeling diode

Connect the RCD suppressor circuit.

### 4) Initial activation of the converter

First switch on the control unit and only afterwards should the mains transformer be switched on.

### 5) Voltage and current measurements

Measure:

5.1) the input voltage  $U_{iAV}$  by the voltmeter P1;

5.2) the input current  $I_{iAV}$  by the ammeter P2;

5.3) the output voltage  $U_{oAV}$  by the voltmeter P3;

5.4) the output current  $I_{oAV}$  by the ammeter P4;

Enter the measured values in the following table.

$U_{iAV} \text{ (V)}$	$I_{iAV} \text{ (A)}$	$U_{oAV} \text{ (V)}$	$I_{oAV} \text{ (A)}$

6) Recording on the oscilloscope

6.1) Recording the  $U_i$  voltage and  $I_i$  current at the input of the converter

Oscilloscope setting

DC coupling; Yt mode. Trigger: EXT.

EXT SYNC input (output  $U_o$  of the converter).

Channel 1 (voltage  $U_i$ )

Channel 2 (current  $I_i$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ )

6.2) Recording the  $U_o$  voltage and  $I_o$  current at the output of the converter

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

EXT SYNC input (output  $U_o$  of the converter).

Channel 1 (voltage  $U_o$ )

Channel 2 (current  $I_o$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ )

7) Control characteristic

The control characteristic  $U_o = f(t_{on})$  at constant load resistance describes the real behaviour of the converter

7.1) Basic settings

7.1.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 3.5 V.

7.1.2) Control unit DL2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 4000 \text{ Hz}$ : coarse adjustment “x100” and fine adjustment “40”.

Inhibit voltage  $U_{INH} = 15 \text{ V}$  (open).

7.1.3) Meters

Set AV/AC+DC measurements for voltmeters P1/P3 and ammeters P2/P4.

Voltmeters P1/P3: measuring range 300 V.

Ammeters P2/P4: measuring range 3 A (1 A).

7.2) Oscilloscope setting

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_o$ )

Channel 2 (current  $I_o$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ )

7.3) Activation of the converter

First switch on the control unit and only afterwards should the mains transformer be switched on.

7.4) Prearrangement

Adjust the scope time base so that only one period of the output voltage is displayed: time base = 25  $\mu\text{s}/\text{div}$ .

If necessary adjust the set point value of the switching frequency  $f = 100 \text{ Hz}$  (fine control) so that the period

$T = 1/f = 250 \mu\text{s}$  covers a screen width of ten divisions and the control voltage  $U_c$  so that the time  $t_{on} = 150 \mu\text{s}$ .

7.5) Reduce the control voltage  $U_c$  in order to carry out the suggested  $t_{on}$  times (measure  $t_{on}$  at the oscilloscope) and enter the measured values in the following table.

$t_{on} (\mu\text{s})$	$U_{iAV} (\text{V})$	$I_{iAV} (\text{A})$	$U_{oAV} (\text{V})$	$I_{oAV} (\text{A})$

Draw the control characteristic  $U_o = f(t_{on})$  of the converter and the curve  $U_i = f(t_{on})$ . Compare measurements with the expected theoretical values.

## 8) Ripple of the output current

Due to the switching operation of the converter the output voltage is comprised of the direct voltage component and the spurious, non-sinusoidal, alternating voltage component. At the output side of the converter the smoothing is carried out by a smoothing inductor connected in series with the load.

### 8.1) Basic settings

Load resistance  $R = 100 \Omega$ .

Filter capacitor  $C = 1000 \mu\text{F}$ .

#### 8.1.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/ $\pm$ 10V) switch on (0/+10V) position.

Set point potentiometer to 3.5 V.

#### 8.1.2) Control unit DL2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 4000 \text{ Hz}$ : coarse adjustment "x100" and fine adjustment "40".

Inhibit voltage  $U_{INH} = 15 \text{ V}$  (open).

#### 8.1.3) Meters

Set AV/AC+DC measurements for voltmeters P1/P3 and ammeters P2/P4.

Voltmeters P1/P3: measuring range 300 V.

Ammeters P2/P4: measuring range 3 A (1 A).

### 8.2) Oscilloscope setting

AC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_o$ )

Channel 2 (current  $I_o$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ )

### 8.3) Activation of the converter

First switch on the control unit and only afterwards should the mains transformer be switched on.

### 8.4) Measurement

Measure the ripple in the output current on the oscilloscope screen.

## EXPERIMENT SIX

### STEP-UP (BOOST) CONVERTER

#### INTRODUCTION

As the name implies this converter produces a greater average output voltage than the dc input voltage. Its main application is in regulated dc power supplies and the regenerative braking of dc motors. The basic circuit is shown in Fig. 1, where the filter capacitor C is assumed to be very large to ensure a constant output voltage value while PWM control is presumed (a switch-on duration  $t_{on} = 100\%$  must be avoided).

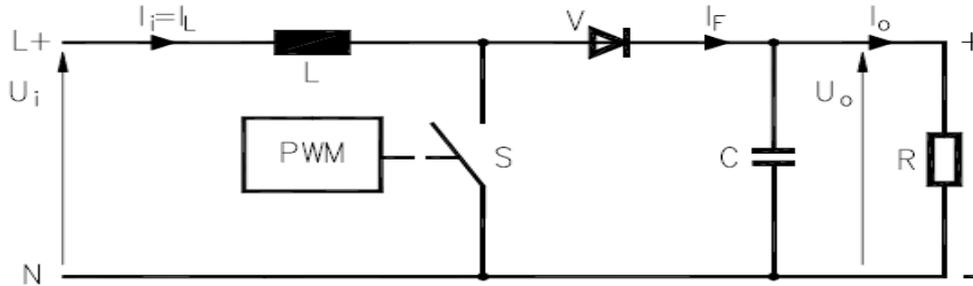


Fig. 1 Step-up (boost) converter

The typical voltage and current characteristics are shown in the following Fig. 2

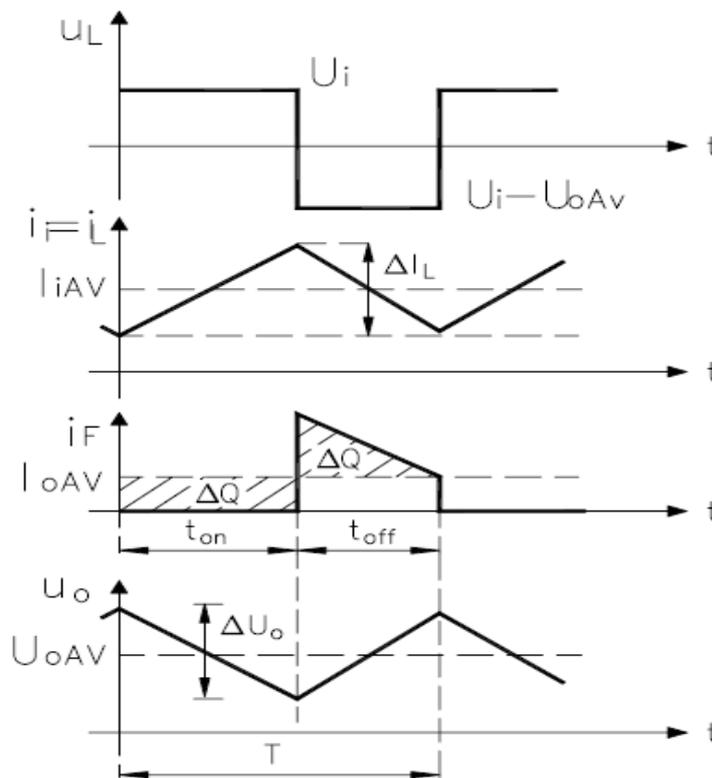


Fig. 2 Voltage and current characteristics, step-up converter

When the switch S is on, the diode V is reverse biased, thus isolating the output stage.

The input supplies energy to the inductor L and causes a linear increase in the inductor current  $I_L$  equal to:

$$(\Delta I_L)_{\text{rising}} = (U_i/L)t_{\text{on}}$$

When the switch S is off, the load receives energy from the inductor L as well as from the input.

This causes a linear decrease of the inductor current equal to:

$$(\Delta I_L)_{\text{falling}} = (U_{oAV} - U_i)t_{\text{off}}/L$$

Since in steady-state operation the variations of current  $I_L$  must be equal, this implies

$$U_{oAV} = U_i(1 + t_{\text{on}}/t_{\text{off}}) = U_i T/t_{\text{off}} = U_i/(1-D)$$

The average value  $I_{oAV}$  of the current flowing through the load R is equal to the average value  $I_{FAV}$  of the diode current. From Fig.2 we observe that

$$I_{FAV} T = I_{iAV} t_{off}$$

So

$$I_{oAV} = I_{iAV} (1-D)$$

The peak-to-peak ripple in the output voltage can be calculated by considering the waveforms shown in Fig.2 for a continuous conduction mode of operation. Assuming that all the ripple component of the diode current  $I_F$  flows through the capacitor C, and its average value flows through the load R, since the shaded area represents the additional charge  $\Delta Q$ , it results

$$\Delta U_o = \Delta Q/C = I_{oAV} t_{on}/C = U_{oAV} DT/(RC) = U_{oAV} D/(fRC)$$

where  $f = 1/T$  is the switching frequency

**Remark**

The conduction mode of the converter can be continuous or discontinuous, based on the inductor current value. Being at the boundary between the continuous and the discontinuous mode, by definition, the inductor current goes to zero at the end of the  $t_{off}$  interval.

At this boundary (subscript B), the average inductor current is:

$$I_{LBAV} = \Delta I_L/2 = U_{oAV} D(1-D)/(2fL)$$

while the corresponding average value of output current is

$$I_{oBAV} = U_{oAV} D(1-D)^2/(2fL)$$


and so, if during an operating condition it results  $I_{oAV} < I_{LBAV}$  (and hence  $I_{LAV} < I_{LBAV}$ ) then the operation will become discontinuous.

# STEP-UP CONVERTER WITH IGBT AND PWM CONTROL

Objectives:

- Measurement and recording of the input and output variables of the converter.
- Control characteristic.

Circuit diagram

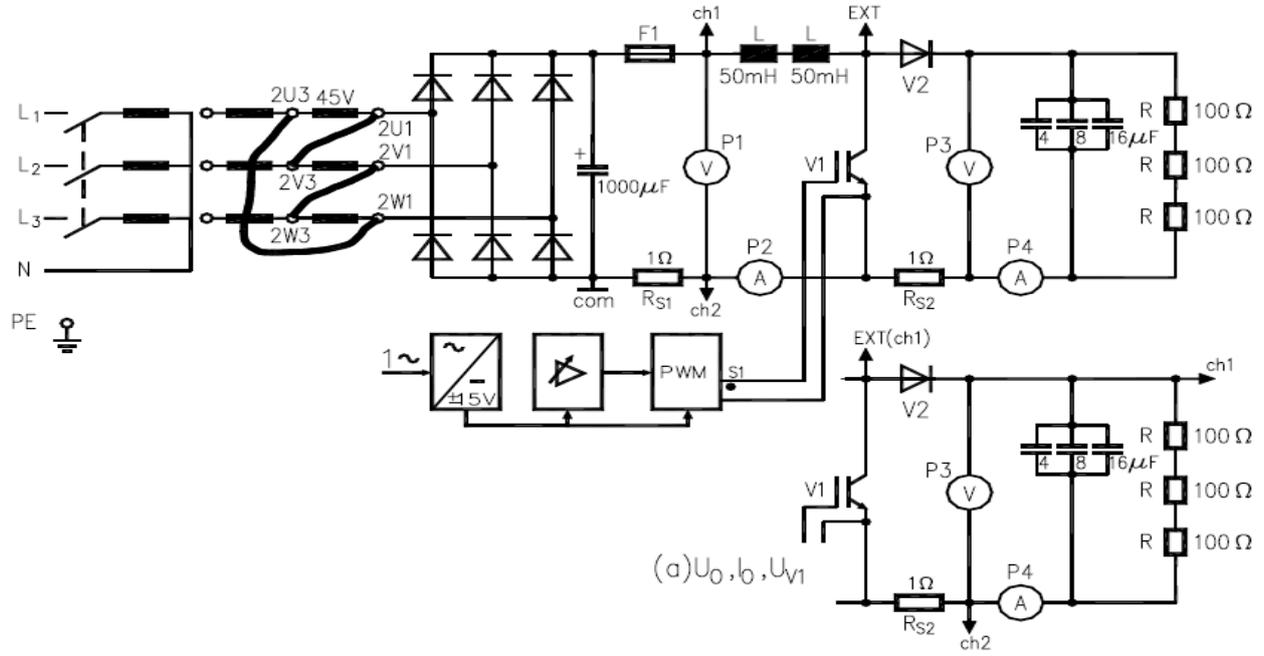

## Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding detail (a) at first.

### 1) Connections

Connect voltage reference generator DL2614 and PWM control unit DL2619 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the pulse output  $S_1$  to gate/emitter circuit of the IGBT  $V_1$ : socket marked with a dot to the gate.

### 2) Preliminary calculations

#### 2.1) Input voltage of the converter

Mesh connected transformer:  $U_v = 45 = 45 \text{ V}$ .

Rectified voltage and dc input voltage of the converter:

$$U_{dAV} = U_{iAV} = 1.35 U_v = 1.35 \times 45 = 60.75 \text{ V}$$

#### 2.2) Input current of the converter

The current on every line supplying the bridge B6U flows for 2/3 of the period and so, being the permissible current  $I_v = 1.5 \text{ A}$  on the secondary phase winding of the mains transformer, the permissible rectified current is

$$I_{dAVmax} = 1.23 \sqrt{3} I_v = 1.23 \times \sqrt{3} \times 1.5 = 3.2 \text{ A}, \text{ but in the presence of the series inductor (} I_{max} = 2.5 \text{ A), the permissible input current of the converter is assumed equal to } I_{iAVmax} = 2.5 \text{ A}$$

#### 2.3) Output voltage of the converter

With the switching frequency  $f = 1000 \text{ Hz}$  and duty ratio  $D = 80\%$  the output voltage is  $60.75/0.2 = 304 \text{ V}$ .

#### 2.4) Output current of the converter; load.

The permissible output current of the converter depends on the permissible current for the relevant used components.

IGBT: 24 A; Load resistance 100  $\Omega$ : 1 A.

The input current of the converter is higher than the output current in accordance with the duty ratio and so, if a load resistance 300  $\Omega$  is assumed the output current is  $304/300 = 1.01 \text{ A}$

### 3) Basic settings

#### 3.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/ $\pm$ 10V) switch on (0/+10V) position.

Set point potentiometer to 0 V.

#### 3.2) Control unit DL2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 1000 \text{ Hz}$ :

Coarse adjustment "x10" and fine adjustment "100".

Inhibit voltage  $U_{INH} = 15 \text{ V}$  (open).

#### 3.3) Meters

Set AV/AC+DC measurements for voltmeters P1/P3 and ammeters P2/P4.

Voltmeters P1/P3: measuring range 300 V (100 V).

Ammeters P2/P4: measuring range 3 A (1 A).

#### 3.4) IGBT

Connect the RCD suppressor circuit.

#### 3.5) Free-wheeling diode

Connect the RCD suppressor circuit.

### 4) Initial activation of the converter

4.1) First switch on the control unit and only afterwards should the mains transformer be switched on.

4.2) As long as the IGBT remains disabled ( $U_c = 0 \text{ V}$ ) the input voltage  $U_i$  feeds the ohmic load via the series inductor and the free-wheeling diode V2.

4.3) Measure and enter the measured values in the following table.

4.3.1) the input voltage  $U_{iAV}$  by the voltmeter P1;

4.3.2) the input current  $I_{iAV}$  by the ammeter P2;

4.3.3) the output voltage  $U_{oAV}$  by the voltmeter P3;

4.3.4) the output current  $I_{oAV}$  by the ammeter P4.

$U_{iAV} \text{ (V)}$	$I_{iAV} \text{ (A)}$	$U_{oAV} \text{ (V)}$	$I_{oAV} \text{ (A)}$

Compare measurements with the expected theoretical values.

5) Increase the control voltage ( $U_c \cong 5 \text{ V}$ ): the converter chops.

Adjust the control voltage and the frequency fine regulation in order to achieve a switching frequency  $f = 1000 \text{ Hz}$  and  $t_{on} = t_{off} = 500 \mu\text{s}$ . Enter the voltage and current measured values in the following table.

$U_{iAV} \text{ (V)}$	$I_{iAV} \text{ (A)}$	$U_{oAV} \text{ (V)}$	$I_{oAV} \text{ (A)}$

6) Recording on the oscilloscope

6.1) Recording the  $U_i$  voltage and  $I_i$  current at the input of the converter

Oscilloscope setting

DC coupling; Yt mode. Trigger: EXT.

EXT SYNC input (voltage  $U_{V1}$  of the IGBT).

Channel 1 (voltage  $U_i$ ): 20 V/div; probe x100.

Channel 2 (current  $I_i$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 0.5 V/div; probe x1.

6.2) Recording the  $U_o$  voltage, and  $I_o$  current at the output of the converter, and the voltage  $U_{V1}$  at IGBT.

Oscilloscope setting:

Assemble the measuring circuit according with detail (a); in order to record the voltage  $U_{V1}$  connect channel 1 to collector of the IGBT corresponding to the EXT SYNC connection.

EXT SYNC input (voltage  $U_{V1}$  of the IGBT).

Channel 1 (voltage  $U_o$ ): 100 V/div; probe x100.

Channel 1 (voltage  $U_{V1}$ ): 100 V/div; probe x100.

Channel 2 (current  $I_o$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 0.5 V/div; probe x1.

7) Control characteristic

7.1) Basic settings:

7.1.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/ $\pm$ 10V) switch on (0/+10V) position.

Set point potentiometer to 5 V.

7.1.2) Control unit DL2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 1000 \text{ Hz}$ :

Coarse adjustment "x10" and fine adjustment "100".

Inhibit voltage  $U_{INH} = 15 \text{ V}$  (open).

7.1.3) Meters

Set AV/AC+DC measurements for voltmeters P1/P3 and ammeters P2/P4.

Voltmeters P1/P3: measuring range 300 V (100).

Ammeters P2/P4: measuring range 3 A (1 A).

7.2) Oscilloscope setting:

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_{V1}$ ): 200 V/div ; probe x100.

Channel 2 (current  $I_o$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 1 V/div ; probe x1.

7.3) Activation of the converter

First switch on the control unit and only afterwards should the mains transformer be switched on.

7.4) Prearrangement

If necessary adjust the set point value of the switching frequency  $f = 100 \text{ Hz}$  (fine control) in order to achieve a switching frequency  $f = 1000 \text{ Hz}$ .

7.5) Adjust the control voltage  $U_c$  in order to carry out the suggested  $t_{on}$  times (measure  $t_{on}$  at the oscilloscope) and enter the measured values in the following table.

$t_{on} \text{ (}\mu\text{s)}$	$U_i \text{ (V)}$	$I_i \text{ (A)}$	$U_o \text{ (V)}$	$I_o \text{ (A)}$

Draw the control characteristic  $U_o = f(t_{on})$  of the converter and the curves  $U_i = f(t_{on})$  and  $I_i = f(t_{on})$   
Compare the measured results with the theoretical predictions.

## EXPERIMENT SEVEN

### SINGLE-PHASE FULLY-CONTROLLED RECTIFIER IN THE INVERSION MODE

#### INTRODUCTION

Fig. 1 shows the fully-controlled bridge rectifier with a supplementary dc voltage  $E_0$  in series with ohmic load.  $E_0$  is in the direction of the direct current  $I_d$ .

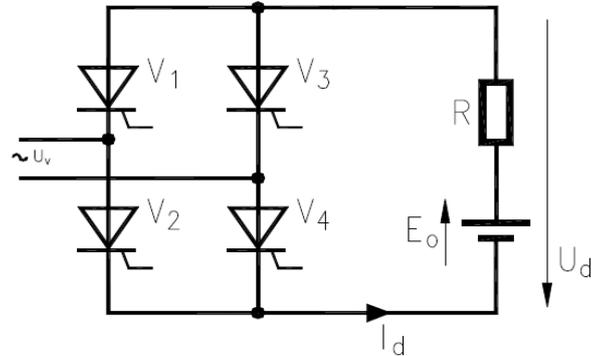


Fig. 1 Controlled rectifier with ohmic load and supplementary dc voltage

With control angle  $0^\circ < \alpha < 90^\circ$  the direct voltage  $U_d$  and supplementary voltage  $E_0$  are in series and a relatively high pulsating output current results: the average direct voltage value is positive.

With control angle  $\alpha > 90^\circ$  the operation is regenerative and the converter works in the inversion mode.

The converter can be continuously controlled from  $\alpha = 0^\circ$  to stability limit while the intermittent operation is avoided because of the sufficiently high supplementary voltage, as shown in Fig. 2.

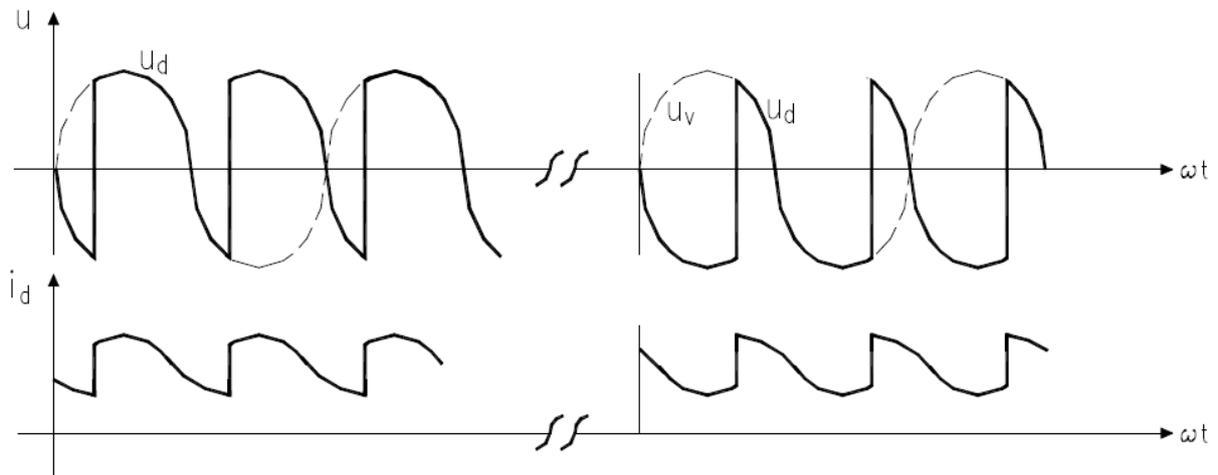


Fig. 2 Voltage and current time profiles

## FULLY-CONTROLLED BRIDGE, DC MOTOR LOAD

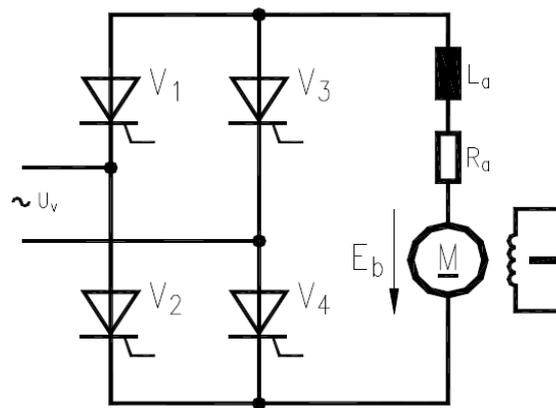


Fig. 3 Fully-controlled bridge, dc motor load

When converter is used in practice, ohmic-inductive load with back-e.m.f.  $E_b$  occurs when operating dc motors:  $E_b$  is an e.m.f. induced in the armature circuit, proportional to the speed,  $R_a$  is the armature winding resistance and  $L_a$  the leakage inductance.

For conducting SCRs the direct voltage follows the time profile of the supply ac voltage while for blocking SCRs the direct voltage is equal to the back-e.m.f., as shown in Fig. 4

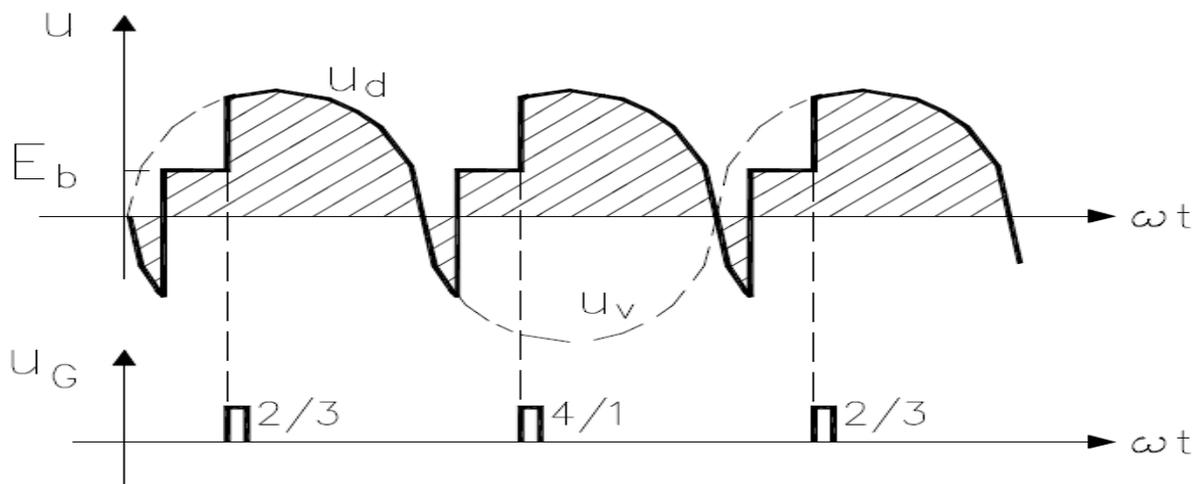


Fig. 4 Voltage time profiles

The SCRs can only be triggered when the instantaneous value of the ac supply voltage is higher than the back e.m.f.: in this case the control range of the converter is limited.

When the SCRs conduct the voltage  $U_d$  is formed from sections of the sinusoidal supply voltage; during the gaps in the current the voltage  $U_d$  is equal to the speed dependent back e.m.f.


The motor inductance is here insufficient to make a continuous load current.

# FULLY-CONTROLLED BRIDGE, OHMIC LOAD AND SUPPLEMENTARY DC VOLTAGE

Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

Circuit diagram

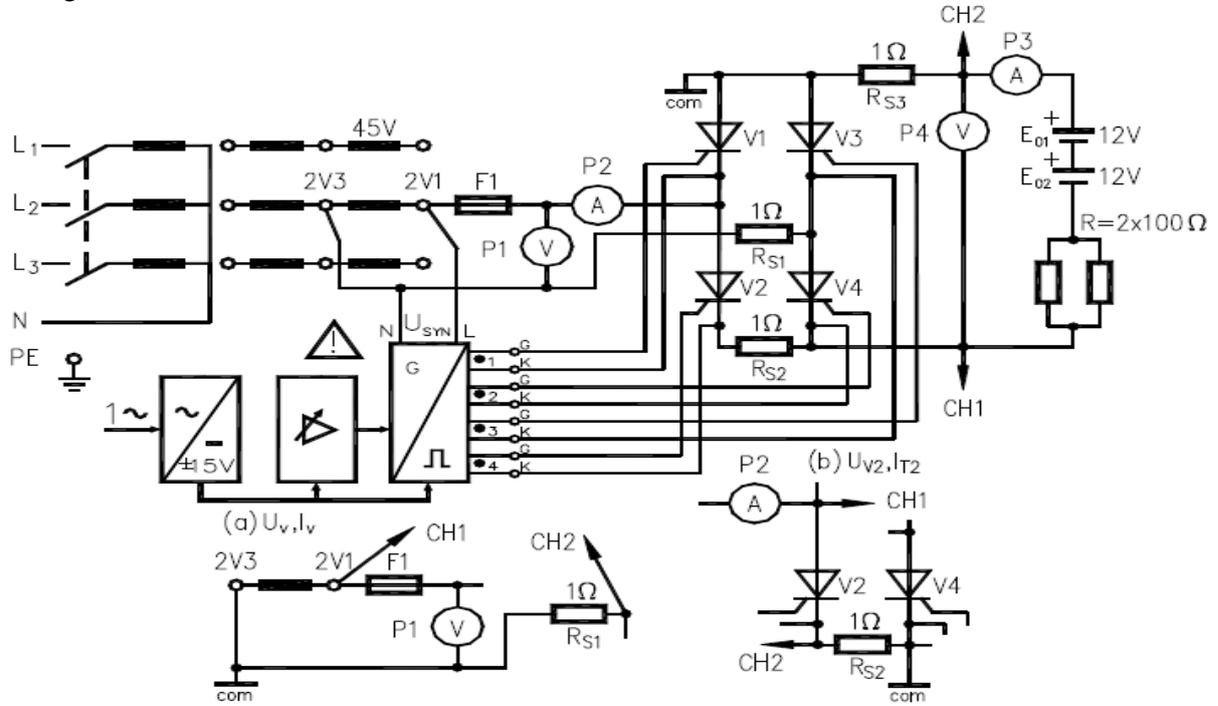

## Experiment Procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding details (a) and (b) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V1/2V3 of the transformer.

Connect the pulse transformers 1, 2 and 3, 4 to gate/cathode circuit of the SCRs  $V_1, V_4$  and  $V_3, V_2$  respectively: socket marked with a dot to the gate.

Connect the Power Analyzer to the input side of the circuit. Ask the instructor to show you how to do this.

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 10 V.

#### 2.2) Control unit DL2616

Control angle  $\alpha_o$  switch on  $0^\circ$  position.

“Pulse shape” switch on pulse train position.

Inhibit voltage UINH = 15 V (open).

### 3) Voltage and current measurements

Supply the circuit and measure:

3.1) the rms value  $U_v$  of the supply voltage by the voltmeter  $P_1$ ;

3.2) the rms value  $I_v$  of the supply current by the ammeter  $P_2$ ;

3.3) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the direct voltage by the voltmeter  $P_3$ ;

3.4) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the direct current by the ammeter  $P_4$ ;

3.5) the average and apparent input power

Enter the measured value as a function of the gate angles  $\alpha$  in the following table.

$\alpha$ ( $^\circ$ )	30	60	120	150
$U_v$ (V)				
$I_v$ (A)				
$U_{dAV\alpha}$ (V)				
$U_{dRMS\alpha}$ (V)				
$I_{dAV\alpha}$ (A)				
$I_{dRMS\alpha}$ (A)				
$P_{in}$ (W)				
S (VA)				

Compare measurements with the expected theoretical values.

### 4) Recording on the oscilloscope ( $\alpha = 60^\circ$ )

#### 4.1) Recording the direct voltage $U_d$ and current $I_d$

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 ( $U_d$  voltage)

Channel 2 (current  $I_d$  proportional to voltage at shunt  $R_{S3} = 1 \Omega$ ): 1 V/div

#### 4.2) Recording the supply voltage $U_v$ and current $I_v$

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

Channel 1 (voltage  $U_v$ )

Channel 2 (current  $I_v$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 1 V/div

#### 4.3) Recording the SCR $V_2$ voltage and current

Oscilloscope setting

Assemble the measuring circuit according with detail (b).

Channel 1 (voltage  $U_{V2}$ )


Channel 2 (current  $I_{T2}$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 1 V/div.

# FULLY-CONTROLLED BRIDGE, DC MOTOR LOAD

## Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

## Circuit diagram

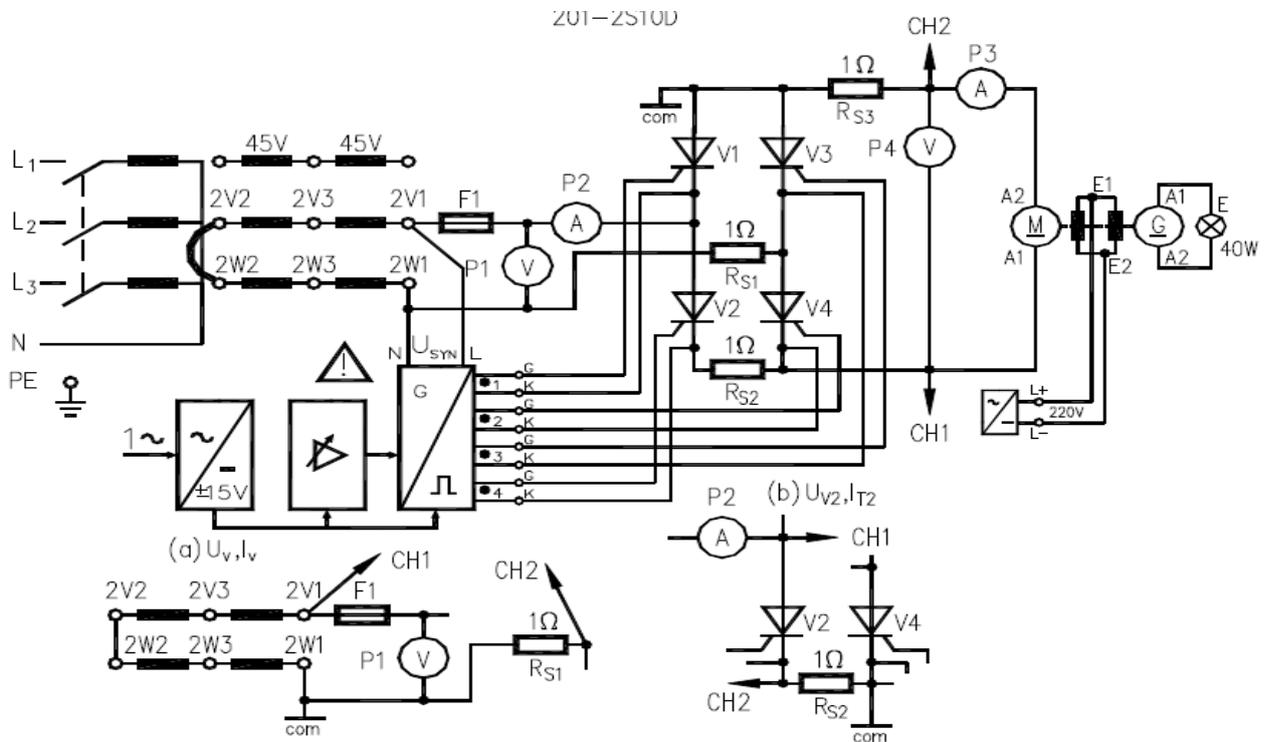

## Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding details (a) and (b) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V1/2W1 of the transformer.

Connect pulse transformers 1, 2 and 3, 4 to gate/cathode circuit of the SCRs  $V_1, V_4$  and  $V_3, V_2$  respectively: socket marked with a dot to the gate.

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 0 V.

#### 2.2) Control unit DL2616

Control angle  $\alpha_o$  switch on  $0^\circ$  position.

“Pulse shape” switch on pulse train position.

Inhibit voltage UINH = 15 V (open).

#### 2.3) Motor

Supply the excitation winding of the machine before to supply the converter.

### 3) Voltage and current measurements

Supply the circuit and measure:

3.1) the rms value  $U_v$  of the supply voltage by the voltmeter P1;

3.2) the rms value  $I_v$  of the supply current by the ammeter P2;

3.3) the average value  $U_{dAV}$  and the rms value  $U_{dRMS}$  of the direct voltage by the voltmeter P3;

3.4) the average value  $I_{dAV}$  and the rms value  $I_{dRMS}$  of the direct current by the ammeter P4.

In addition measure the rotational frequency  $n$ .

Enter the measured value as a function of the gate angles in the following table.

$\alpha$ ( $^\circ$ )	60	90
$U_v$ (V)		
$I_v$ (A)		
$U_{dAV\alpha}$ (V)		
$U_{dRMS\alpha}$ (V)		
$I_{dAV\alpha}$ (A)		
$I_{dRMS\alpha}$ (A)		
$n$ ( $\text{min}^{-1}$ )		

With control angle  $\alpha < 60^\circ$  the converter operation becomes unstable (pulsating motor speed).

### 4) Recording on the oscilloscope ( $\alpha = 90^\circ$ )

4.1) Recording the direct voltage  $U_d$  and current  $I_d$ . Oscilloscope setting:

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 ( $U_d$  voltage): 100 V/div, probe x100.

Channel 2 (current  $I_d$  proportional to voltage at shunt  $R_{S3} = 1 \Omega$ ): 500 mV/div, probe x1.

4.2) Recording the supply voltage  $U_v$  and current  $I_v$ .

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

Channel 1 (voltage  $U_v$ ): 100 V/div; probe x100.

Channel 2 (current  $I_v$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 1 V/div; probe x1.

## EXPERIMENT EIGHT

### SINGLE-PHASE SWITCHED-MODE INVERTER

#### INTRODUCTION

Inverters are converters used to convert the dc input into a sinusoidal ac output with variable frequency and amplitude. Dc-to-ac inverters are used in ac-motor drives and uninterruptible ac power supplies. To be precise, the switch-mode inverter is a converter through which the power flow is reversible.

Let us consider a single-phase inverter, which is shown in block-diagram form in Fig.1, where the input voltage is assumed to be a dc voltage  $U_d$  source and the output voltage  $U_o$  is filtered so that it can be assumed to be sinusoidal.

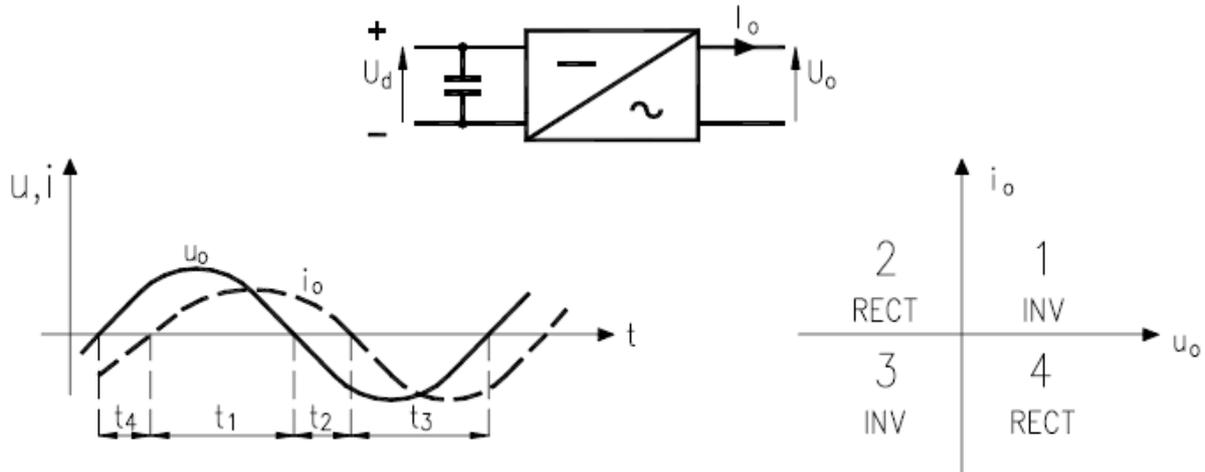


Fig. 1 Single-phase inverter block diagram and filtered output waveforms

The output waveforms show that during the intervals  $t_1$  and  $t_3$  the instantaneous power  $p_o = u_o i_o$  is positive and therefore it flows from the dc side to the ac side (inverter operation); in contrast, during the intervals  $t_2$  and  $t_4$  the power is negative and therefore it flows from the ac side to the dc side (rectifier operation).

A step-down converter is only suitable for single-quadrant operation.

A half-bridge circuit can be used to reverse the current if an active load is involved.

A genuine four-quadrant operation can be achieved with the help of a full-bridge: due to arrangement of their components, full-bridge is often termed H-bridge.

#### Single-phase half-bridge inverter

Figure 2 shows the basic half-bridge inverter, where we assume that the input dc voltage  $U_d$  is constant and that the potential at midpoint "O" remains essentially constant with respect to the negative dc bus N.

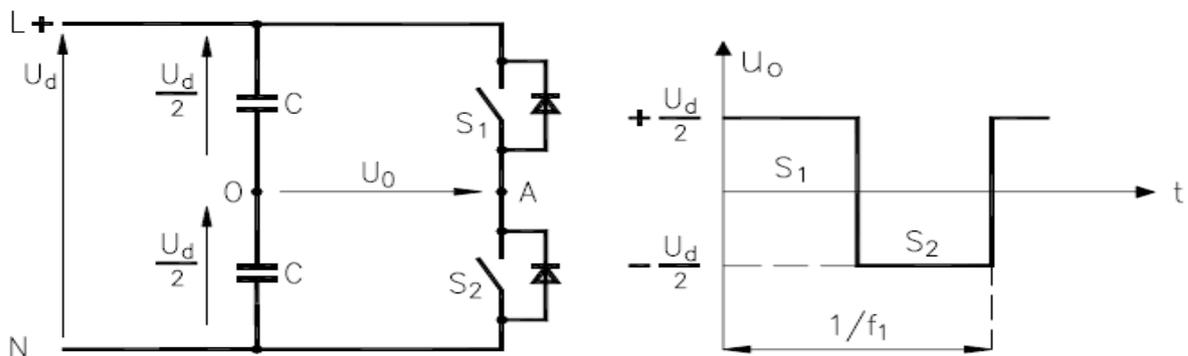


Fig. 2 Single-phase half-bridge inverter and output voltage waveform

Since the two switches  $S_1$  and  $S_2$  are never off simultaneously, the output voltage  $U_o$  fluctuates between the following values dictated by the switch states:

$U_d/2$  (  $S_1$  on,  $S_2$  off )

$-U_d/2$  (  $S_1$  off,  $S_2$  on )

When the switch  $S_1$  is on the output current will flow through  $S_1$  and the point A is at positive potential  $U_d$ .

Similarly when the switch  $S_2$  is on the output current will flow through  $S_2$  and the point A is at zero potential. In the square-wave switching mode, each switch is on for one-half cycle ( $180^\circ$ ) of the desired frequency  $f_1$  of the output sinusoidal voltage. From Fourier analysis of the output voltage waveform the peak values of the fundamental frequency  $f_1$  and that of the harmonic components  $f_h$  ( $h$  takes only odd values) can be obtained. In order to produce a sinusoidal output voltage waveform at a desired fundamental frequency  $f_1$  it is necessary that the control signal of PWM switching be sinusoidal at the frequency  $f_1$ .

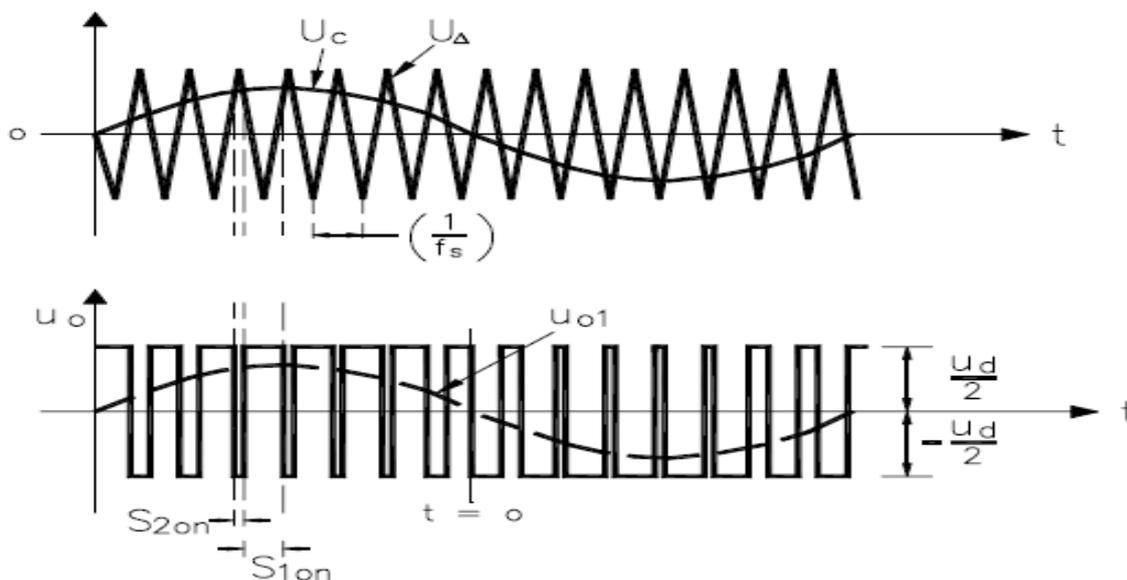


Fig. 3 Single-phase inverter output with sinusoidal PWM

The frequency of the triangular waveform establishes the inverter switching frequency  $f_s$  while the control voltage  $U_c$  is used to modulate the switch duty cycle.

The inverter output voltage will not be a perfect sine wave and will contain voltage components at harmonic frequencies of  $f_1$ .

The harmonic spectrum of the output voltage depends on the amplitude modulation ratio  $m_a$  and on the frequency modulation ratio  $m_f$

The peak amplitude of the fundamental frequency component is ( $m_a \leq 1$ )

The harmonics in the output voltage appear as sidebands centered around the switching frequency and its multiples.

The frequency modulation ratio  $m_f$  should be an odd integer so only odd harmonics are present.

In most applications, the switching frequency  $f_s$  is selected to be either less than 6 kHz or greater than 20 kHz to be above the audible range.

**Remark**

The two switches are switched in such a way that when one of them is in its off state, the other switch is on: in practice they are both off for a short time interval (blanking time) to avoid short-circuit of the dc input.

### Single-phase full-bridge inverter

A full-bridge inverter consists of two half-bridge inverters, as shown in the following Fig.4: with the same dc input voltage, the maximum output voltage is twice that of the half-bridge inverter.

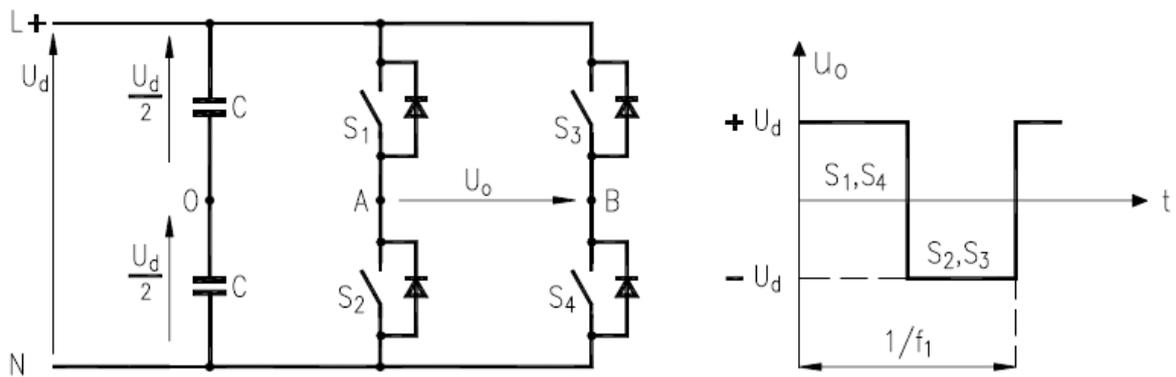


Fig. 4 Single-phase full-bridge (H-bridge) inverter and output voltage waveform

In this scheme, the diagonally opposite switches ( $S_1, S_4$ ) and ( $S_2, S_3$ ) are switched simultaneously and so, carrying out the same analysis as the half-bridge inverter, the output voltage fluctuates between the following values dictated by the switch states:

$$\begin{aligned}
 U_d & \quad (S_1 \text{ \& } S_4 \text{ on, } S_2 \text{ \& } S_3 \text{ off}) \\
 -U_d & \quad (S_1 \text{ \& } S_4 \text{ off, } S_2 \text{ \& } S_3 \text{ on})
 \end{aligned}$$

In the square-wave switching mode, each pair switch is on for one-half cycle ( $180^\circ$ ) of the desired frequency  $f_1$  of the output sinusoidal voltage.


When sinusoidal PWM switching is used the same results apply as explained earlier. The output voltage, however, is twice that of the half-bridge inverter.

# SINGLE-PHASE FULL-BRIDGE INVERTER WITH SINUSOIDAL PWM CONTROL

Objectives:

- Production of a sinusoidal voltage.
- Measurement and recording of the input and output variables of the inverter.

Circuit diagram

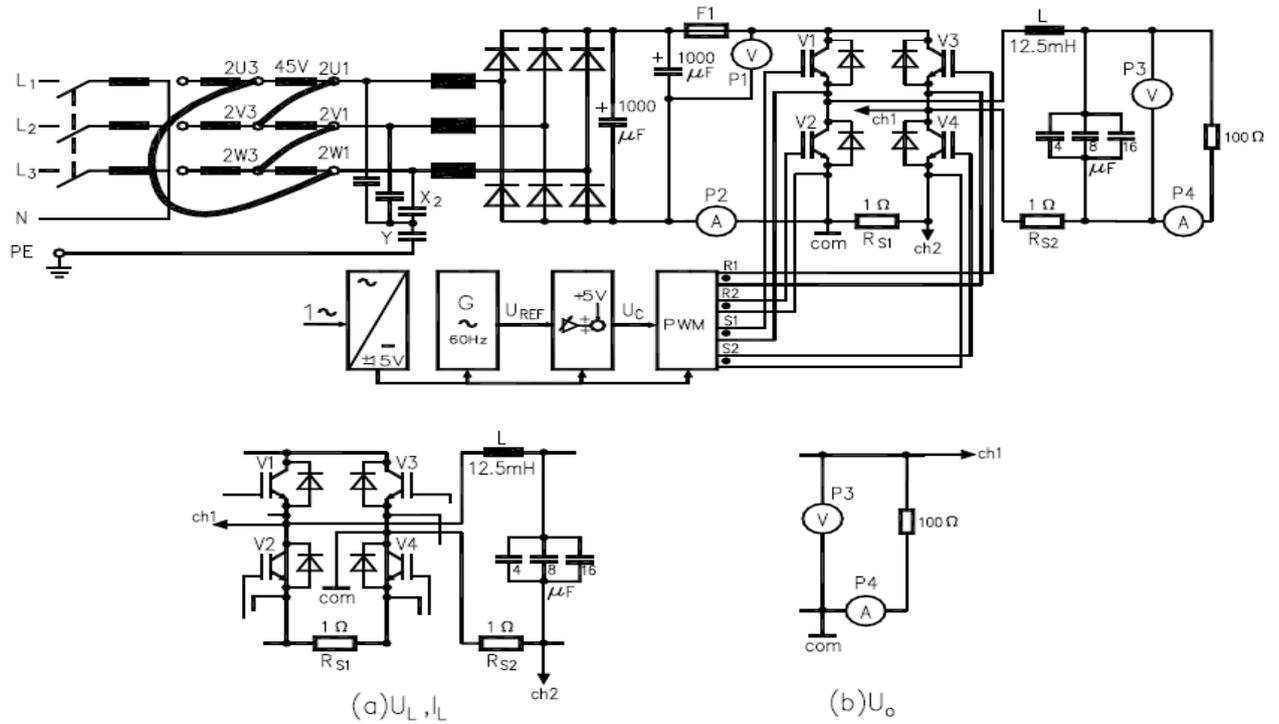

## Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding details (a) and (b) at first. Before you connect the function generator, the matching amplifier and control unit follow steps from 1) to 3).

### 1) Auxiliary power supply

Connect the function generator DL2633 and the matching amplifier DL2625 to the power supply +15V/0/-15V. At the moment do not supply the PWM control unit DL2619.

### 2) Basic settings

#### 2.1) Function generator DL2633

Function: sinusoidal wave.

Signal frequency  $f = 60$  Hz: coarse adjustment "x10" and fine adjustment "6".

LEVEL potentiometer to 50%.

Connect the output  $U_o$  to the input  $U_i$  of the matching amplifier.

#### 2.2) Matching amplifier DL2625

Arrange the offset function: offset switch on "offset on" position and offset potentiometer to +5 V approx.

Amplification: gain = 0.5x1.

Time constant:  $\tau = 0$ .

Do not connect the output  $U_o$  to the input  $U_c$  of the PWM unit.

#### 2.3) Control unit DL2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 2$  kHz:

coarse adjustment "x10" and fine adjustment "200" approx.

Inhibit voltage  $U_{INH} = 15$  V (open).

Connect the pulse outputs  $S_1$ - $S_2$  and  $R_1$ - $R_2$  to gate/emitter circuit of the IGBTs  $V_1$ - $V_4$  and  $V_2$ - $V_3$  respectively: socket marked with a dot to the gate.

#### 2.4) Meters

Set AV/AC+DC measurements for meters  $P_1/P_2$  and RMS/AC+DC measurements for meters  $P_3/P_4$ .

Voltmeters  $P_1/P_3$ : measuring range 100 V.

Ammeters  $P_2/P_4$ : measuring range 1 A.

### 3) Pre-arrangement of the control voltage of PWM unit.

The control unit PWM processes voltages in the range 0...+10 V so the control voltage must be matched conveniently.

3.1) Recording the reference voltage  $U_{REF}$  at the output of the function generator and the control voltage  $U_c$  at the output of the matching amplifier: use an oscilloscope.

Oscilloscope setting:

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_{REF}$ ): 10 V/div; probe x10.

Channel 2 (voltage  $U_c$ ): 2 V/div; probe x1.

Common: 0 V.

3.2) Switch on the auxiliary power supply and the function generator.

Adjust the frequency  $f = 60$  Hz (fine control) and the amplitude  $U_{REF} = 16$  Vpp (LEVEL potentiometer) of the square wave.

Adjust the control signal  $U_c$  at the output of the matching amplifier:

offset potentiometer ( $U_c = 5$  VMEAN):

amplification "gain" ( $U_c = 8$  Vpp).

3.3) Switch off the auxiliary power supply.

### 4) Connections

Complete the connections connecting the output  $U_o$  of the amplifier to input  $U_c$  of the control unit PWM.

Connect the control unit PWM to the power supply +15V/0/-15V.

5) Initial activation of the inverter.

5.1) First switch on the control unit and only afterwards should the mains transformer switched on.

5.2) Recording the  $U_{V4}$  voltage and  $I_{T4}$  current at the IGBT  $V_4$ .

Oscilloscope setting:

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_{V4}$ ): 50 V/div; probe x10.

Channel 2 (current  $I_{T4}$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 2 V/div; probe x1.

If necessary adjust the set point value of the switching frequency  $f = 2 \text{ kHz}$  (fine control).

6) Recording on the oscilloscope

6.1) Recording the  $U_L$  voltage across the bridge diagonal and the  $I_L$  inductor current.

Oscilloscope setting

Assemble the measuring circuit according with detail (a).

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_L$ ): 50 V/div; probe x10.

Channel 2 (current  $I_L$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 2 V/div; probe x1.

6.2) Recording the  $U_o$  voltage at the output of the inverter.

Oscilloscope setting

Assemble the measuring circuit according with detail (b).

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_o$ ): 20 V/div; probe x10.

The output voltage results in a sinusoidal characteristic with frequency equal to the reference signal frequency. The ripple of the output voltage depends on the filtration effect: the higher the capacitance the lower the voltage ripple. The higher the switching frequency the lower the ripple.

### Note

*Owing to the circuit unavoidable dissymmetry it is possible that the output voltage contains a dc component. You can perform any necessary adjustment using the offset control on the matching amplifier to maintain the dc component at a zero value.*

7) Voltage and current measurements

$U_i(\text{V})$	
$I_i(\text{A})$	
$U_o(\text{V})$	
$I_i(\text{A})$	

8) Use the digital oscilloscope to perform FFT on the output voltage  $U_o$ . Plot the harmonic spectrum and make a record of your observations.

## EXPERIMENT NINE

### SINGLE-PHASE AC VOLTAGE CONTROLLER

#### INTRODUCTION

The continuous control of alternating electrical energy is normally performed by means of thyristors that are suitable for use as static switches on account of their extremely high switching capacity.

The thyristor family includes unidirectional devices as the SCRs and bidirectional devices as the TRIACs. As a switch conducts current in both directions so two SCRs must always be connected back-to-back (pair of anti-parallel arms) while the TRIAC can be used instead of the two anti-parallel SCRs. A TRIAC can be considered as two parallel SCRs oriented in opposite directions and integrated into a semiconductor chip to provide symmetrical bidirectional characteristics.

#### SINGLE-PHASE AC CONTROLLER

The simplest device used to continuously adjust the ac power is shown in the following Fig.1, where two anti-parallel SCRs can be used instead of the TRIAC.

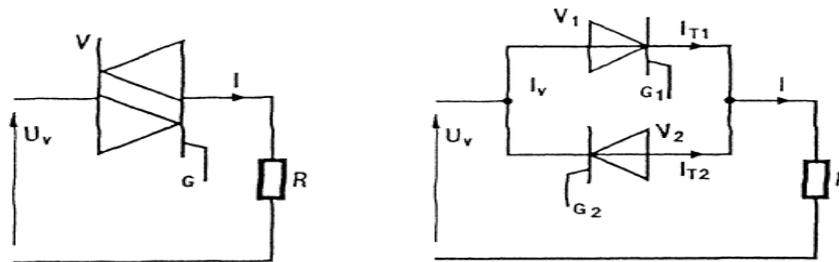


Fig. 1 Single-phase AC controller, ohmic load

The power regulation is accomplished by varying the control angle  $\alpha$  of the TRIAC (of the two SCRs) during each half-period, as shown in the following Fig.2.

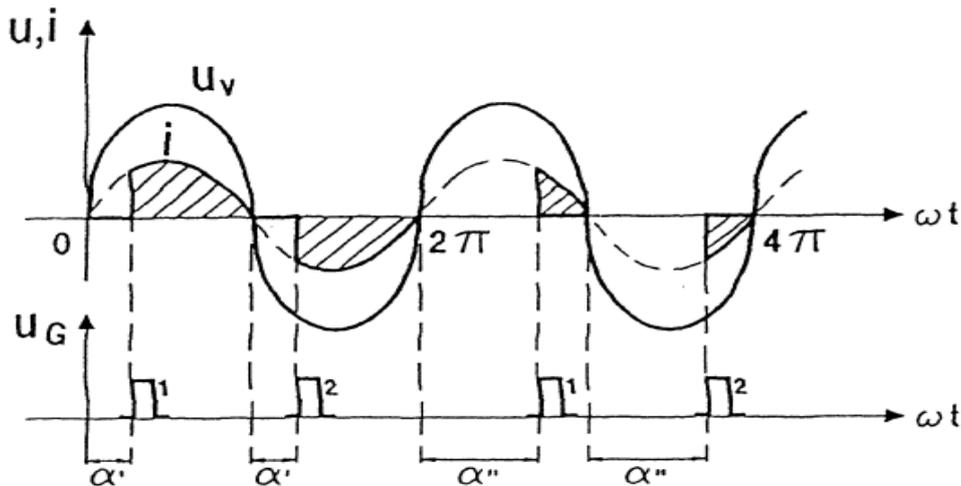


Fig.2 Voltage and current profiles

In the case of an ohmic load, the load current rises to the instantaneous value of the sinusoidal continuous current at the moment of firing angle and then flows in phase with the sinusoidal supply voltage until the zero transition is reached.

The load current can be continuously varied via the control angle  $\alpha$  between the maximum value ( $\alpha = 0^\circ$ ) and zero ( $\alpha = 180^\circ$ ).

During the conduction phase the supply voltage is connected to the load; during the off-phase it is present at the controller as a reverse voltage.

All the following characteristics values apply to resistive load, neglecting losses in the controller.

Average value of SCR current

$$I_{TAV} = U_{vM}(1+\cos\alpha)/(2\pi R)$$

Rms value of SCR current

$$I_{TRMS} = (U_{vM}/R)[(\pi-\alpha+0.5\sin 2\alpha)/(4\pi)]^{0.5}$$

Rms value of load current

$$I_{RMS} = (2)^{0.5}(I_{TRMS}) = (U_{vM}/R)[(\pi-\alpha+0.5\sin 2\alpha)/(2\pi)]^{0.5}$$

The power transfer characteristic reflects the relationship between the load active power  $P$  and control angle  $\alpha$ , as illustrated in Fig.3, where  $P_o = U^2_v/R$  is the full drive power for the gate control angle  $\alpha = 0^\circ$ .

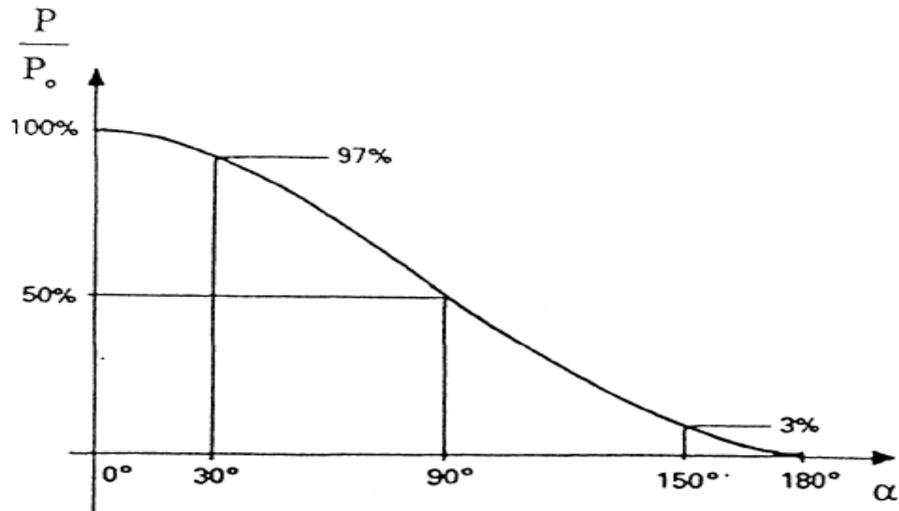


Fig. 3 Power transfer characteristics, AC controller with ohmic load

In addition the power factor PF on the supply side is

$$PF = P/S = P/(U_v I)$$

and results inductive even in circuits with ohmic load.

**Ohmic-inductive load**

Circuits containing resistance and inductance in series are a load type frequently found in practice.

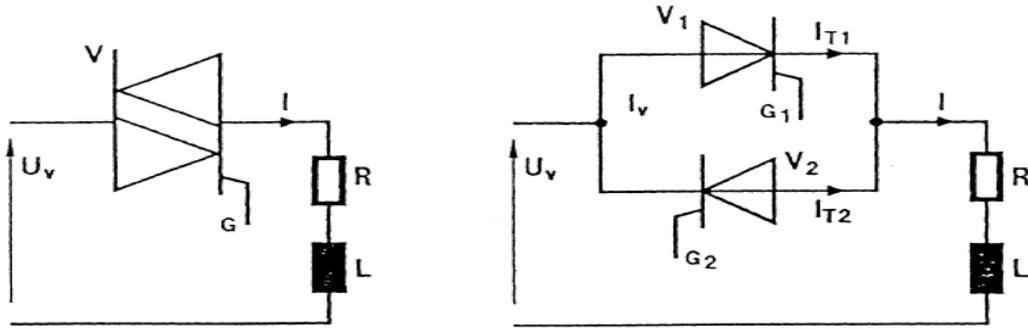


Fig. 4 Single-phase AC controller, ohmic-inductive load

The ohmic-inductive load represents a load case between ohmic and purely inductive load. Full drive is obtained when  $\alpha = \varphi = \arctan(\omega L/R)$  and so the controller control range is between  $\alpha = \varphi$  and  $180^\circ$ .

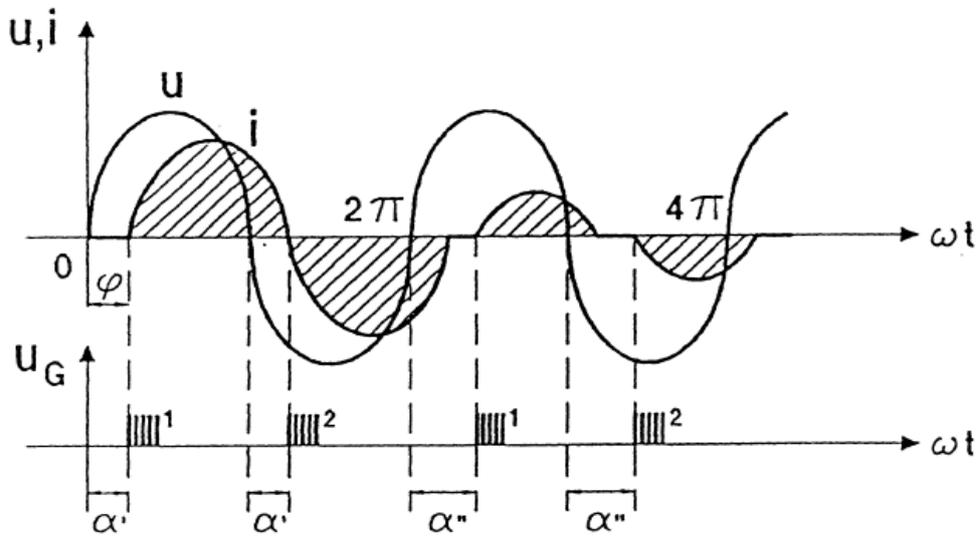


Fig.5 Voltage and current profiles


The load current is no longer sinusoidal but is made up of sinusoidal continuous current and superimposed equalizing current decreasing with the time constant  $\tau = L/R$ . During the conduction phase the supply voltage is connected to the load; during the off-phase it is present at the controller as a reverse voltage.

# SINGLE-PHASE AC CONTROLLER, OHMIC-INDUCTIVE LOAD

## Objectives:

- Recording voltage and current time profiles
- Voltage and current measurements
- Determination of various characteristic data

## Circuit diagram

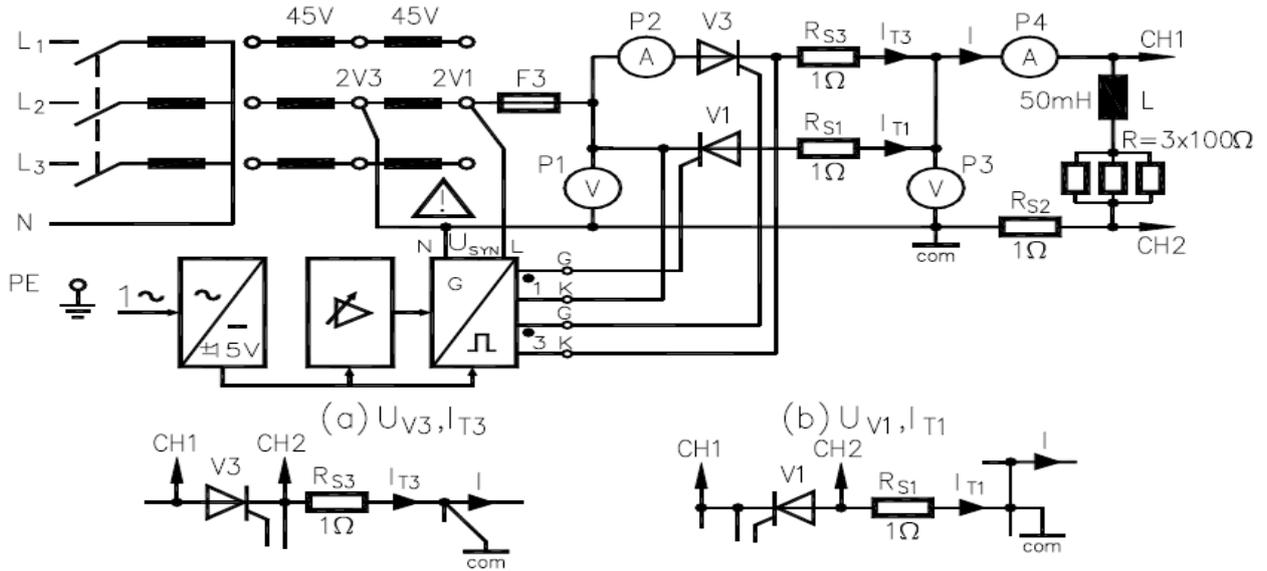

## Experiment procedure

Assemble the circuit according with the foregoing topographic diagram, disregarding details (a) and (b) at first.

### 1) Connections

Connect the voltage reference generator DL2614 and control unit DL2616 to the power supply +15V/0/-15V.

Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit.

Connect the terminals L/N ( $U_{SYN}$ ) of the control unit respectively to terminals 2V1/2V3 of the transformer.

Connect the pulse transformers 1 and 3 to gate/cathode circuit of the SCRs  $V_1$  and  $V_3$  respectively: socket marked with a dot to the gate.

### 2) Basic settings

#### 2.1) Voltage reference generator DL2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position.

Set point potentiometer to 0 V.

#### 2.2) Control unit DL2616

Control angle  $\alpha_o$  switch on  $0^\circ$  position.

“Pulse shape” switch on train pulse position.

Inhibit voltage  $U_{INH} = 15$  V (open).

### 3) Voltage and current measurements

Supply the circuit and measure:

3.1) the rms value  $U_v$  of the supply voltage by the voltmeter  $P_1$ ;

3.2) the average value  $I_{T3AV}$  and the rms value  $I_{T3RMS}$  of the SCR  $V_3$  current by the ammeter  $P_2$ .

3.3) the rms value  $U_{RMS}$  of the load voltage by the voltmeter  $P_3$ ;

3.4) the rms value  $I_{RMS}$  of the load current by the ammeter  $P_4$ .

Enter measured values as a function of the gate angle  $\alpha$  in  $30^\circ$  steps between  $0^\circ$  and  $180^\circ$  in the following table.

**Control range:** Load current lags behind the voltage by an angle  $\varphi = \arctan(\omega L/R)$  and for this reason the controller can only be controlled between  $\varphi$  and  $180^\circ$ .

Increase the control voltage  $U_c$  until the oscilloscope shows the load voltage  $U$  and current  $I$  in a sinusoidal continuous form; at this point slowly decrease the control voltage  $U_c$  until the oscilloscope shows the full drive of both SCRs at the gate angle corresponding to the load phase angle  $\varphi$ .

$\alpha$ ( $^\circ$ )	$\varphi$	30	60	90	120	150	180
$U_{v\alpha}$ (V)							
$U_{RMS\alpha}$ (V)							
$I_{RMS\alpha}$ (A)							
$I_{T3AV\alpha}$ (A)							
$I_{T3RMS\alpha}$ (A)							

Evaluate the various characteristic data of the controller and compare these with the theoretical values.

### 4) Recording on the oscilloscope ( $\alpha = 90^\circ$ )

#### 4.1) Recording the load $U$ voltage and $I$ current.

Oscilloscope setting

DC coupling; Yt mode. Trigger: AC Line.

Channel 1 (voltage  $U$ ): 50 V/div; probe x10.

Channel 2 (current  $I$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 2 V/div; probe x1.

#### 4.2) Recording the SCR $V_3$ voltage $U_{V3}$ and current $I_{T3}$ .

Oscilloscope setting:

Assemble the measuring circuit according with detail (a).

Channel 1 ( $U_{V3}$  voltage): 50 V/div; probe x10.

Channel 2 (current  $I_{T3}$  proportional to voltage at shunt  $R_{S3} = 1 \Omega$ ): 2 V/div; probe x1.

#### 4.3) Recording the SCR $V_1$ voltage $U_{V1}$ and current $I_{T1}$ .

Oscilloscope setting:

Assemble the measuring circuit according with detail (b).

Channel 1 ( $U_{V1}$  voltage): 50 V/div; probe x10.


Channel 2 (current  $I_{T1}$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 2 V/div; probe x1

## EXPERIMENT TEN

### FLYBACK CONVERTER


#### INTRODUCTION

The basic circuit of the flyback converter is shown in the following Fig.1.

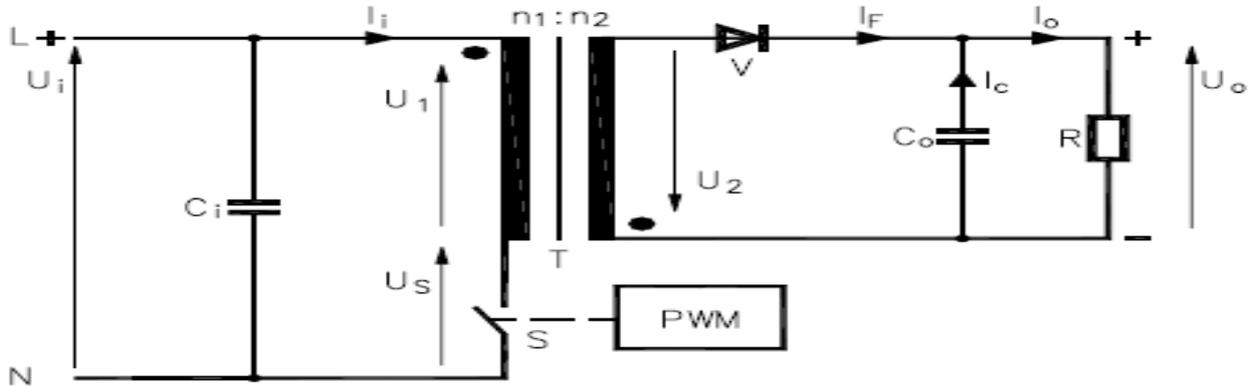

**Fig.1 Flyback converter**

When the switch S is ON, energy is stored in the primary of the transformer (primarily in the air gap of the ferrite core) while the diode V is reverse biased, the capacitor  $C_o$  discharges into the load R. When the switch S is turned off the voltage across the secondary winding rises until the diode V becomes conductive and therefore the energy stored in the transformer causes the current to flow in the secondary and consequently the capacitor  $C_o$  recharges. The magnetizing current  $I_m$  can have continuous (flyback with trapezoid characteristic) or discontinuous (flyback with triangular characteristic) flow depending on the control or the transformer load. Figure 2 shows the steady-state waveforms for continuous flow where the magnetic current  $I_m$  flows continuously.

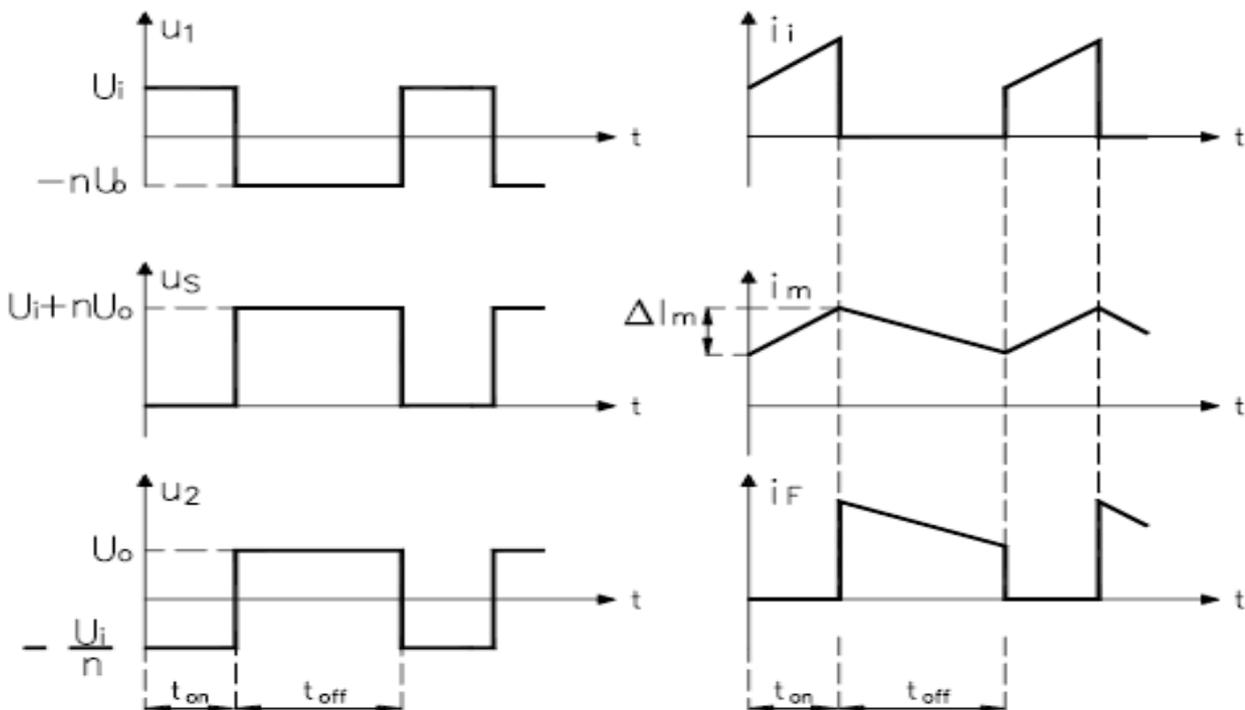

**Fig.2 Flyback converter waveforms**

During the  $t_{on}$  period the primary winding conducts the magnetization current that shows a linear increase equal to

$$\Delta I_m = (U_i/L_1)t_{on}$$

where  $L_1$  is the inductance of the primary winding.

When the switch S is turned off the voltage across the windings reverses and it results

$$u_2 = U_o + U_F \cong U_o$$
$$u_1 = -nU_o$$

where  $n = n_1/n_2$  is the transformer ratio.

During the  $t_{off}$  period the magnetization current has a linear decrease equal to

$$\Delta I_m = (nU_o/L_1)t_{off}$$

Since in the steady-state operation the variations of the current  $I_m$  must be equal, this implies

$$(U_i/L_1)t_{on} = (nU_o/L_1)t_{off}$$

and so

$$U_{oAV} = (U_i/n)(t_{on}/t_{off}) = U_i(n_2/n_1)(D/(1-D))$$

where  $D = t_{on}/T$  is the duty cycle

The output voltage changes when the duty cycle is changes and approaches infinity as  $D = 1$ . This must be prevented by means of a suitable control.

The voltage across the switch during the off interval is


$$U_s = U_i + nU_o = U_i/(1-D)$$

## FLYBACK CONVERTER WITH IGBT (PWM CONTROL)

Objectives:

- Measurement and recording of the input and output variables of the converter.
- Control characteristic.

Circuit diagram

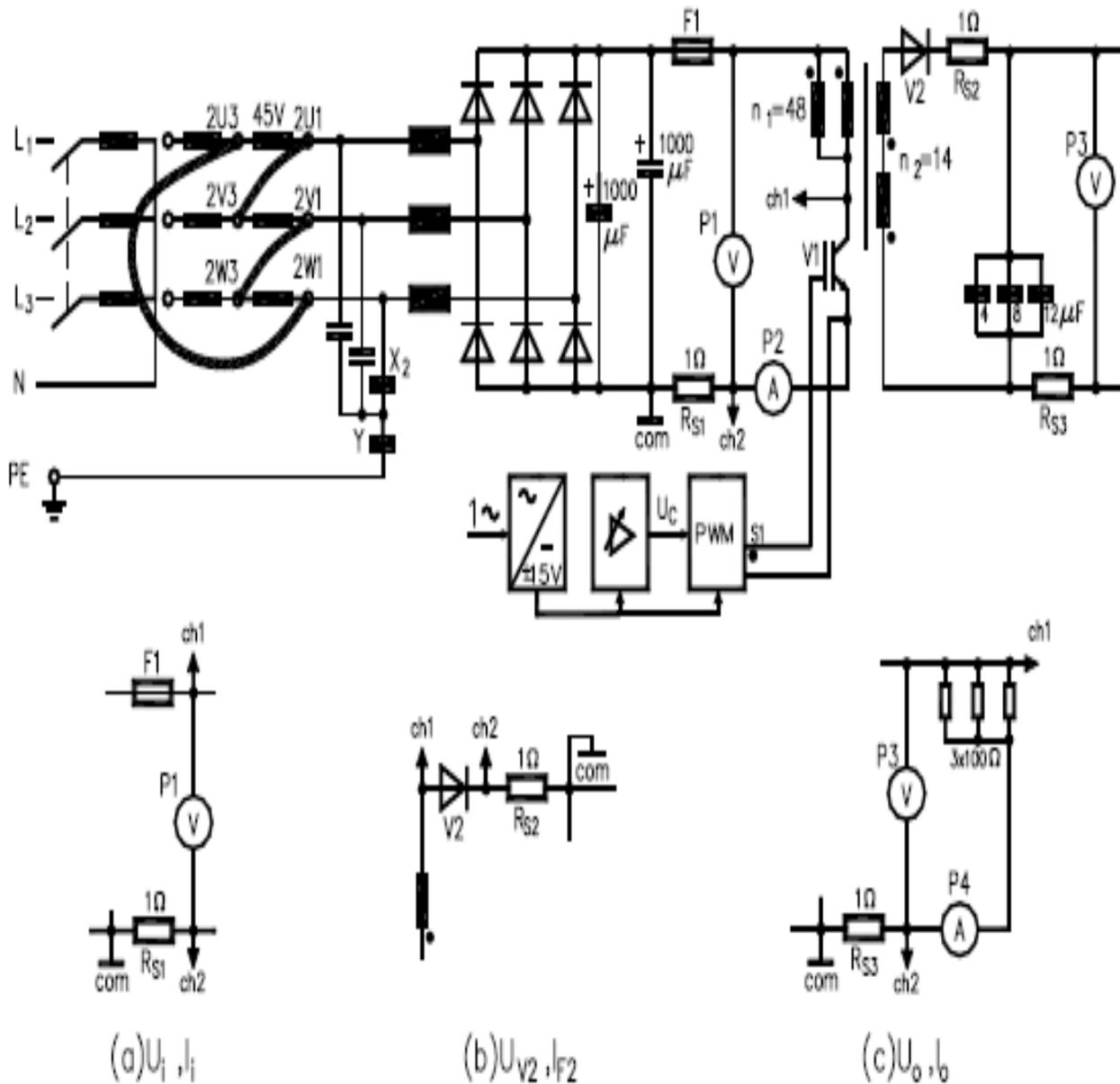

### Experiment procedure

Assemble the circuit according to the foregoing circuit diagram, with the load being three 100  $\Omega$  resistors in parallel. Use an external DC power supply instead of the rectified mains.

#### 1) Connections

Connect the voltage reference generator DL2614 and PWM control unit DL2619 to power supply +15V/0/-15V. Connect the output  $U_o$  of voltage generator to input  $U_c$  of the control unit. Connect the pulse output  $S_1$  to gate/emitter circuit of the IGBT  $V_1$ : socket marked with a dot to the gate.

## 2) Basic settings

### 2.1) Voltage reference generator DL 2614

EXT/INT switch on INT position

(0/+10V)/(0/±10V) switch on (0/+10V) position

Set point potentiometer to 0 V.

### 2.2) Control unit DL 2619

Connect the PWM output to input  $U_i$  of the output amplifier.

Switching frequency  $f = 15$  kHz:

Coarse adjustment “x100”, and fine adjustment “150” approx.

Inhibit voltage  $U_{INH} = 15$  V (open).

### 2.3) Meters

Set AV/AC+DC measurements for voltmeters P1/P3 and ammeters P2/P4.

Voltmeters P1/P3: measuring range 100 V (30 V).

Ammeters P2/P4: measuring range 1 A (0.3 A).

### 2.4) IGBT

Connect the RCD suppressor circuit.

### 2.5) Silicon diode

Do not connect the RCD suppressor circuit

3) Initial activation of the converter:

3.1) First, switch on the control unit and only afterwards should the mains transformer be switched on.

3.2) Increase slowly the control voltage  $U_c = 4$  V approx.

#### **Warning**

Do not exceed the  $U_c = 5$  V value otherwise the switching transformer core becomes magnetically saturated: this reduces the inductance so that the current rises and triggers the thermal protection of the transformer.

The switching transformer used in this experiment allows the transmission of low power levels as it is designed and optimized for forward converters and only achieves its rated performance with them: nevertheless, the operating principle of the flyback converter can be demonstrated.

Voltage and current measurements

Measure:

4.1) the input voltage  $U_{iAV}$  by the voltmeter P1;

4.2) the input current  $I_{iAV} = I_{T1}$  by the ammeter P2;

4.3) the output voltage  $U_{oAV}$  by the voltmeter P3;

4.4) the output current  $I_{oAV}$  by the ammeter P4.

Enter the measured values in the following table.

$U_{iAV}$ (V)	$I_{iAV}$ (A)	$U_{oAV}$ (V)	$I_{oAV}$ (A)

## 5) Recording on the oscilloscope

#### **Note**

*Since the basic instrument set does not normally allow simultaneous measurements, the measures may have to be carried out successively.*

### 5.1) Recording the $U_{V1}$ voltage and $I_i$ current at the IGBT

Oscilloscope setting:

DC coupling; Yt mode. Trigger: Ch2.

Channel 1 (voltage  $U_{V1}$ ): 50 V/div; probe x100.

Channel 2 (current  $I_i$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 2 V/div; probe x1.

### 5.2) Recording the $U_i$ voltage and $I_i$ current at the input of the converter

Oscilloscope setting:

Assemble the measuring circuit according with detail (a).

DC coupling; Yt mode. Trigger: Ch2.

Channel 1 (voltage  $U_i$ ): 50 V/div; probe x100.

Channel 2 (current  $I_i$  proportional to voltage at shunt  $R_{S1} = 1 \Omega$ ): 2 V/div; probe x1.

5.3) Recording the  $U_{V2}$  voltage and  $I_{F2}$  current at the diode  $V_2$

Oscilloscope setting:

Assemble the measuring circuit according with detail (b).

DC coupling; Yt mode. Trigger: Ch2.

Channel 1 (voltage  $U_{V2}$ ): 20 V/div; probe x100.

Channel 2 (current  $I_{F2}$  proportional to voltage at shunt  $R_{S2} = 1 \Omega$ ): 2 V/div; probe x1.

5.4) Recording the  $U_o$  voltage and  $I_o$  current at the output of the converter

Oscilloscope setting:

Assemble the measuring circuit according with detail (c).

DC coupling; Yt mode. Trigger: Ch1.

Channel 1 (voltage  $U_o$ ): 5 V/div; probe x100.

Channel 2 (current  $I_o$  proportional to voltage at shunt  $R_{S3} = 1 \Omega$ ): 1 V/div; probe x1.

## 6) Control characteristics

With  $U_i = 66 \text{ V}$  and  $T = 66 \mu\text{s}$ , adjust the control voltage  $U_c$  in order to obtain the tabulated values (reading on graduated scale) and enter the measured values in the following table (measure  $t_{on}$  on the oscilloscope).

Draw the control characteristics  $U_o = f(D)$  of the converter and the curve  $I_i = f(D)$ .

$U_c$ (V)	$t_{on}$ ( $\mu\text{s}$ )	D	$I_{iAV}$ (A)	$U_{oAV}$ (V)	$I_{oAV}$ (A)
1.5	11	0.166			
2	16	0.242			
2.5	17	0.257			
3	20	0.3			
3.5	24	0.364			
4	26	0.394			
4.5	37	0.56			


## EXPERIMENT 11

### Generation of electric energy from photovoltaic panels and its inlet in the mains network


Photovoltaic (PV) cells work according to a basic physical phenomenon called ‘photoelectric effect’. When the energy of photons hitting a semiconductor plate is high enough it can be absorbed by electrons on the surface of the semiconductor plate exposed to such radiation. The absorption of additional energy enables the (negatively charged) electrons to set free from their atoms. The electrons become mobile, and the space which is left behind is filled by another electron from a deeper part of the semiconductor. As a consequence, one side of the wafer (thin slice of a semiconductor material) has a higher concentration of electrons than the other, which creates a voltage between the two sides. Joining the two sides with an electrical wire enables the electrons to flow to the other side of the wafer which is electrical current. PV modules built from PV cells have humble efficiency of approx. 15%.

#### Characteristics of a solar cell

A solar cell is defined by its  $I$ - $V$  curve. A typical  $I$ - $V$  characteristic of the cell for a certain irradiation  $G$  and a certain fixed temperature  $T$  is shown in Fig. 1. For a resistive load, the load characteristic is a straight line with slope  $I/V=1/R$ . the power delivered to the load depends on the value of the resistance only. However, if the load  $R$  is small, the cell operates in the region M-N of the curve where the cell behaves as a constant current source, almost equal to the short circuit current  $I_{SC}$ . On the other hand, if  $R$  is large, the cell operates on the regions P-S of the curve, the cell behaves more as a constant voltage source, almost equal to the open-circuit voltage  $V_{OC}$ .

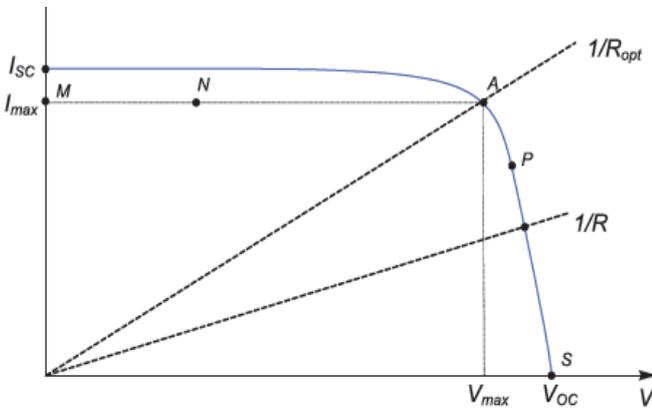

**Fig.1**

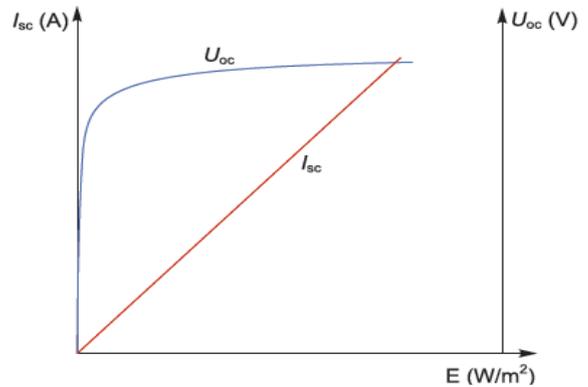

**Fig.2**

A real solar cell can be characterized by the following fundamental parameters, sketched in Fig. 1:

- Short-circuit current  $I_{SC}$  is the greatest value of current generated by a cell. It is produced when voltage is  $V = 0$ .
- Open-circuit voltage  $V_{OC}$  corresponds to the voltage when the cell current is  $I = 0$ .

$$V_{oc} = \frac{kT}{e} \ln \left( \frac{I_{sc}}{I_o} + 1 \right)$$

Where  $k$  is the Boltzmann constant ( $1.38 \times 10^{-23} \text{ J/}^\circ\text{K}$ ), and  $T$  is the temperature ( $^\circ\text{K}$ ),  $e$  is electron charge ( $1.6 \times 10^{-19} \text{ Coul.}$ ), and  $I_o$  is the saturation current (A)

- Maximum power point is the operating point marked A in the figure, where  $P_{max} = V_{max} \cdot I_{max}$
- Maximum efficiency is the ratio between the maximum power and the incident light power.

$$\eta = \frac{P_{max}}{P_{in}} = \frac{I_{max} V_{max}}{A G_a}$$

Where  $G_a$  is the irradiation and  $A$  is the cell area

- Fill factor is the ratio of the maximum power that can be delivered to the load and the product of  $I_{SC}$  and  $V_{OC}$

$$FF = \frac{P_{max}}{V_{oc} I_{sc}} = \frac{I_{max} V_{max}}{V_{oc} I_{sc}}$$

The fill factor is a measure of the real  $I$ - $V$  characteristic. Its value is higher than 0.7 for good-quality cells. The fill factor diminishes as cell temperature is increased. The open circuit voltage increases logarithmically with the irradiation, while the short circuit current is a linear function of the irradiation, as shown in Fig. 2. The dominant effect with increasing cell's temperature is the linear decrease of the open circuit voltage, the cell being thus less efficient. The short circuit current increases with the cell temperature.

## Irradiation and Temperature Measurements

**Required equipment:** Solar panel, DC power source (DL9032), solar panel measuring unit (DL9021)

### Exercise 1: Setting the solar panel to the most irradiated position

1. Connect the module according to Fig. 3.
2. Find the position in which the solar panel provides highest irradiation using the built-in angle-meter.
3. Read the solar panel temperature.

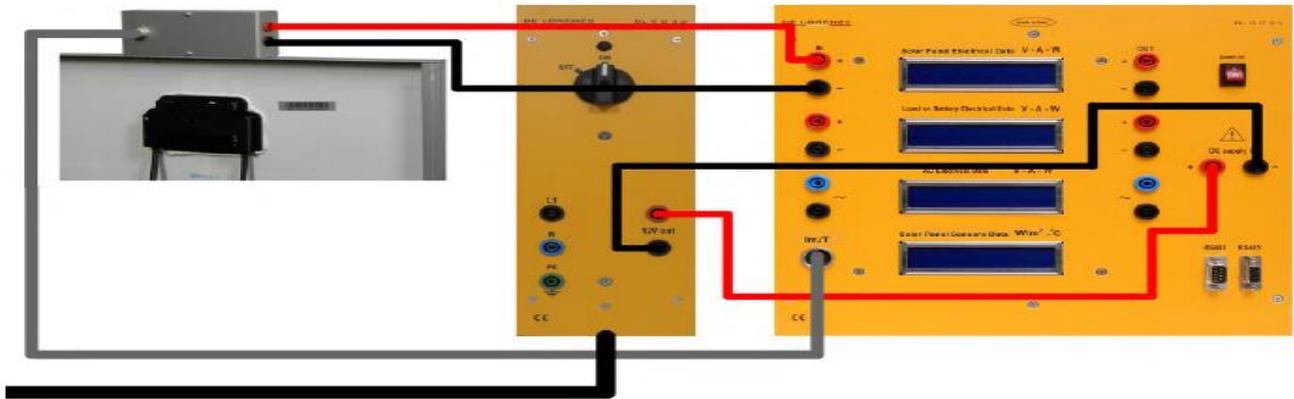


Fig. 3

### Exercise 2: Changing the inclination of the solar panel

1. Change the inclination of the solar panel and fill in the following table.
2. Draw the inclination/irradiation graph based upon measurements.

Inclination (°)	0	10	20	30	40	50	60	70	80	90
Irradiation (W/m <sup>2</sup> )										

## Solar Panel Voltage-Irradiation Curve, Current-Irradiation Curve and Resistance of the Solar Panel

### Exercise 1: Obtaining the solar panel voltage-irradiation curve

1. Connect the module according to the Fig. 3.
2. Find the position in which the solar panel provides highest irradiation using the built-in angle-meter.
3. Change the inclination and direction of the solar panel in order to obtain at least 8 different irradiation values (between zero and maximum irradiation value). Fill in the output voltage of the panel for each of them in the table.
4. Draw the voltage-irradiation graph.
5. Find the position in which the solar panel provides highest irradiation again.
6. Measure the open-circuit voltage.

Irradiation (W/m <sup>2</sup> )										
Voltage (V)										

### Exercise 2: Calculating the inner resistance of the solar panel

1. Connect the module according to Fig.3.
2. Find the position in which the solar panel provides highest irradiation using the built-in angle-meter
3. Change the inclination and direction of the solar panel in order to obtain at least 8 different irradiation values (between zero and maximum irradiation value). Fill in the short-circuit current of the panel for each in the table.
4. Draw the current-irradiation graph.
5. Find the position in which the solar panel provides highest irradiation again.
6. Measure the short-circuit current.
7. Using the open-circuit voltage from point 6 of the previous exercise, calculate the solar panel inner resistance.

Irradiation (W/m <sup>2</sup> )										
Resistance (Ω)										

## Current-Voltage Characteristics of the Solar Panel

**Required equipment:** Solar panel, DC power source DL9032, rheostat DL9018, panel measuring unit DL9021

### Exercise: Obtaining the solar panel current-voltage curve

The circuit diagram of this exercise is provided in Fig. 4, while Fig. 5 provides a detailed circuit.

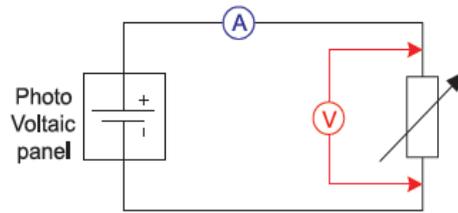


Fig. 4

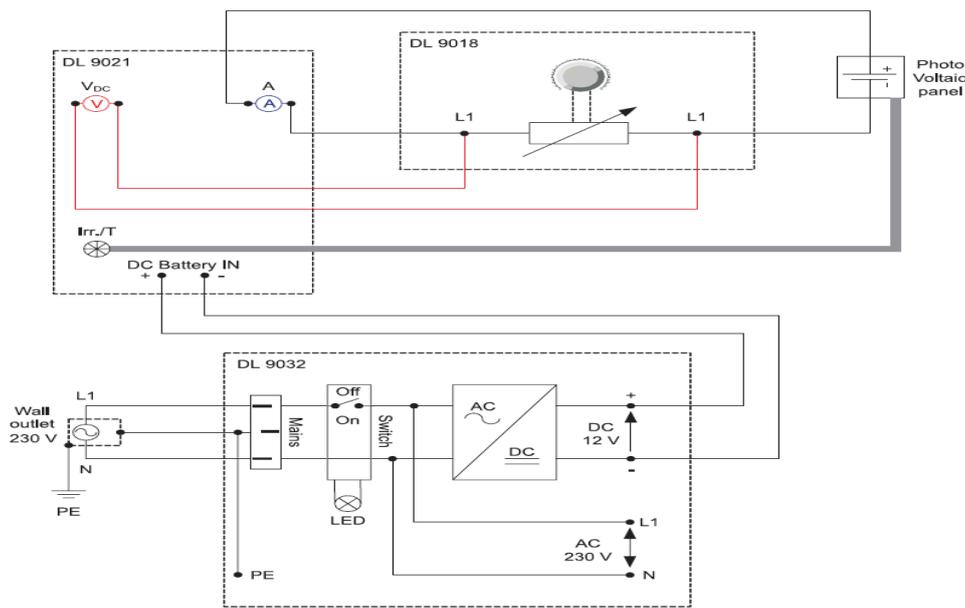


Fig. 5

Connect the modules according to Fig. 5

1. Find the position in which the solar panel provides highest irradiation using the built-in angle-meter.
2. Set the rheostat to the maximum resistance position.
3. Fill in the values of voltage and current into the table.
4. Lower the resistance of the rheostat to app. 90% and fill in the values of voltage and current into the table.
5. Repeat point 4 in 10% steps until reaching the minimum resistance position of the rheostat.
6. Change the inclination and direction of the solar panel in order to obtain app. 75% of the maximum irradiation. Repeat the procedure described in points 2-5.
7. Change the inclination and direction of the solar panel in order to obtain app. 50% of the maximum irradiation. Repeat the procedure described in points 2-5.
8. Change the inclination and direction of the solar panel in order to obtain app. 25% of the maximum irradiation. Repeat the procedure described in points 2-5.
9. Draw the current-voltage graph for all 4 irradiation scenarios.

Resistance of the Rheostat (% of the maximum value)	100	90	80	70	60	50	40	30	20	10	0
Current (A)											
Voltage (V)											

## Solar Panel Electricity Delivered to the Mains Grid

### DL9013G grid tie power inverter

The main difference between a standard power inverter and a grid tie power inverter is that the latter also ensures that the power supplied will be in phase with the grid power. This allows individuals with surplus power (wind, solar, etc.) to sell power back to utility in the form of net metering or the arrangement local power utility offers. The traditional grid tie inverters are in the high output, about 1-10 kW, they are very heavy and expensive. Therefore, most people interested in green energy generation cannot afford it. DL9013G micro grid tie inverter is very economical, easy to install, convenient and reliable. DL9013G has 12 V solar panel input, ground terminal and AC terminals. Power grid voltage should be connected to “Mains” terminals to ensure that power supplied will be in phase with grid. “Mains” terminals should also be connected to the load (lamp for example) that is supposed to be powered from solar panel connected to the PV input. Power inverter in module DL9013G is programmed to supply load from PV source and surplus energy is sent to the grid. If PV source cannot produce enough energy for the load, then mains grid supplies the load. The result is that the load is always supplied with electrical energy. If “Mains” terminals are disconnected from power grid then Island Protection LED glows red.

### Required equipment

Solar panel, DC power source (DL9032), protective module (DL9031), solar panel measuring unit (DL9021), grid tie power inverter (DL9013G), AC measurement module (DL9030)

### Exercise: Measuring the electricity delivered to the mains grid

The circuit diagram of this exercise is provided in Fig. 6.

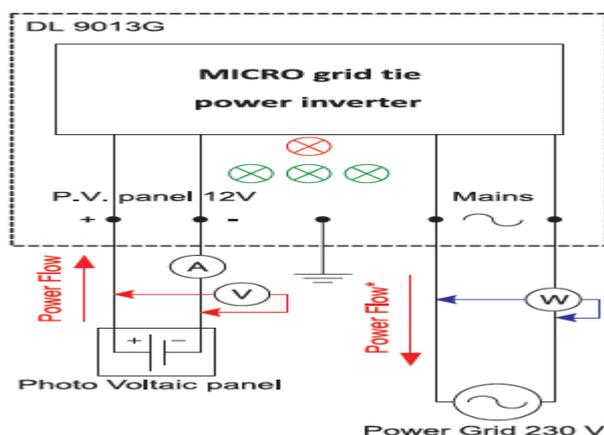


Fig. 6

Connect the modules according to Fig. 6.

1. Find the position in which the solar panel provides highest irradiation.
2. Using DL9030 read the value of electricity being delivered to the mains grid.
3. Fill in this value into the table.
4. Set the panel such that irradiation is app. 90% of its highest value and fill in the appropriate row in the table.
5. Repeat point 4 in 10% steps until reaching the minimum irradiation is reached, i.e. 0 W/m<sup>2</sup>
6. Draw the delivered electricity-irradiation graph.

Irradiation (W/m <sup>2</sup> )											
Current (A)											
Voltage (V)											
Delivered Power (W)											

## Solar Panel Supplying Load

### Required equipment

Solar panel, DC power source (DL9032), protective module (DL9031), solar panel measuring unit (DL9021), loads module (DL9017), grid tie power inverter (DL9013G), AC measurement module (DL9030)

### Exercise 1: Measuring the electricity produced by the solar panel and delivered/taken from the mains

The circuit diagram of this exercise is provided in Fig. 7.

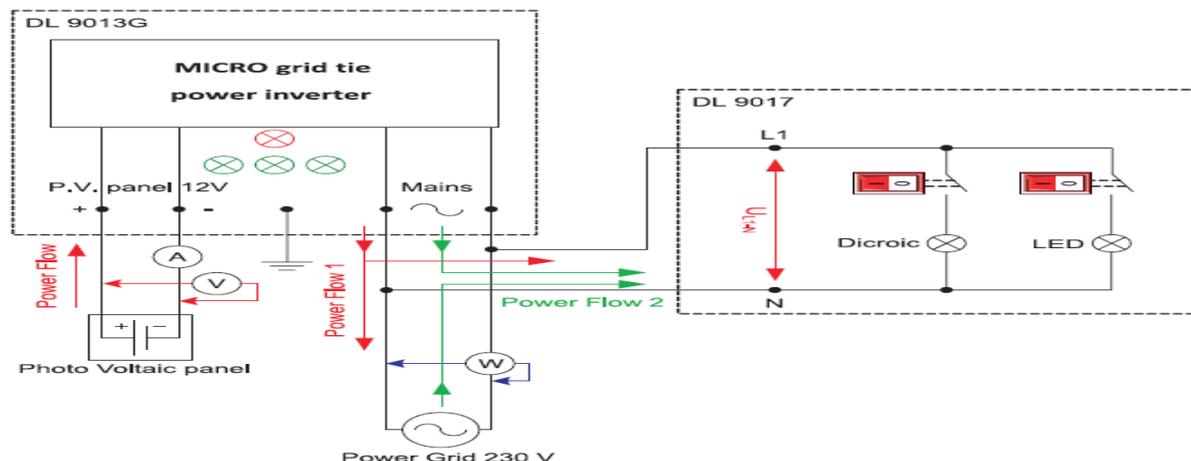


Fig. 7

Connect the modules according to Fig. 7.


1. Find the position in which the solar panel provides highest irradiation.
2. Switch on the LED lamp on DL9017 module.
3. Use DL9021 to read the power produced by the panel and DL9030 to read the power being delivered to the grid.
4. Fill in the produced and delivered electricity values in case of LED lamp turned on in first row of the table.
5. Switch off the LED lamp and turn on the dichroic lamp on DL9017 module.
6. Use DL9021 to read the power produced by the panel and DL9030 to read the power being delivered to the grid.
7. Fill in the produced and delivered electricity values in case of dichroic lamp turned on in first row of the table.
8. Switch on both the LED lamp the dichroic lamp on DL9017 module.
9. Use DL9021 to read the power produced by the panel and DL9030 to read the power being delivered to the grid.
10. Fill in the produced and delivered electricity values in case of both LED lamp and dichroic lamp turned on in first row of the table.
11. Set the panel such that irradiation is app. 90% of its highest value and fill in the appropriate row in the table.
12. Repeat points 2-10 in 10% steps until reaching the minimum irradiation is reached, i.e. 0 W/m<sup>2</sup>.
13. Draw the produced electricity-irradiation and delivered electricity-irradiation graphs for all three cases.

*Note: DL9021 contains AC wattmeter, and solar panel produced DC power. Therefore, we cannot measure the solar panel power directly. The power is calculated by multiplying voltage and current measured with DL9021 module.*

Irradiation (W/m <sup>2</sup> )	LED lamp		Dichroic lamp		LED and Dichroic	
	Produced electricity (W)	Delivered electricity (W)	Produced electricity (W)	Delivered electricity (W)	Produced electricity (W)	Delivered electricity (W)

**Exercise 2: Measuring the electricity produced by the solar panel, delivered/taken from the mains grid, and the loading of DL9017 lamps**

The circuit diagram of this exercise is provided in Fig. 8.

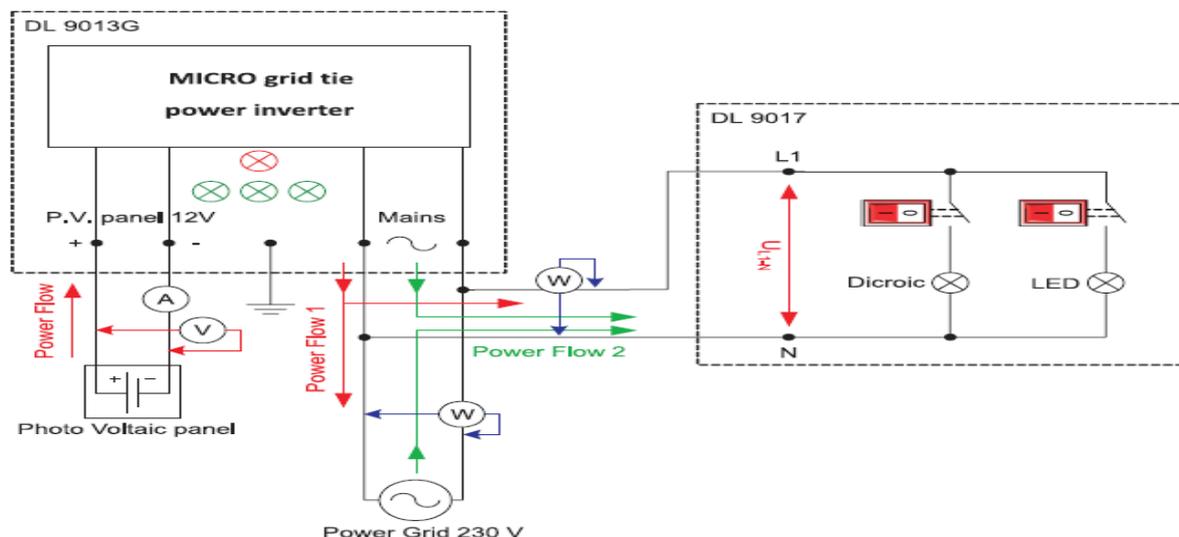

**Fig. 8**

Connect the module according to Fig. 8.

1. Find the position in which the solar panel provides highest irradiation.
2. Switch on the LED lamp on DL9017 module.
3. Use DL9021 to calculate the power produced by the panel (use ammeter and voltmeter), and to read the value of DL9017 loading. Use DL9030 to read power delivered to the grid.
4. Fill in the table the produced electricity, loading value and delivered electricity to the grid in case of LED lamp turned on
5. Switch off the LED lamp and turn on the dichroic lamp on DL9017 module.
6. Use DL9021 to calculate the power produced by the panel (use ammeter and voltmeter), and to read the value of DL9017 loading. Use DL9030 to read the power delivered to the grid.
7. Fill in the table the produced electricity, loading value and delivered electricity to the mains grid in case of dichroic lamp turned on
8. Switch on both the LED lamp the dichroic lamp on DL9017 module.
9. Use DL9021 to calculate the value of power produced by the solar panel (use ammeter and voltmeter), and to read the value of DL9017 loading. Use DL 9030 to read the value of power delivered to the grid.
10. Fill in the produced electricity, loading value and delivered electricity to the grid in case of both LED lamp and dichroic lamp turned on in the table.
11. Set the panel such that irradiation is app. 90% of its highest value and fill in the appropriate row in the table.
12. Repeat points 2-10 in 10% steps until reaching the minimum irradiation is reached, i.e. 0 W/m<sup>2</sup>.
13. Draw the produced electricity - irradiation, delivered electricity - irradiation and loading - irradiation graphs for all three cases.

Irradiation (W/m <sup>2</sup> )	LED lamp			Dichroic lamp			LED and Dichroic		
	Produced electricity (W)	Loading (W)	Delivered electricity (W)	Produced electricity (W)	Loading (W)	Delivered electricity (W)	Produced electricity (W)	Loading (W)	Delivered electricity (W)